



ELECTRONIC CIRCUITS - I

lab Manual (EC-261)

Prepared By:

T SRINIVASA RAO M.Tech

SUNEEL MIRIYALA M.Tech.

N.Kusuma DECE.

Y.V.Krishna DECE.

Department of ECE

BAPATLA ENGINEERING COLLEGE

(Autonomous)

BAPATLA-522 101

LIST OF EXPERIMENTS

1. Half Wave Rectifier with and without Filters.
2. Full Wave Rectifier with and without Filters.
3. Bridge Rectifier With and Without Filters.
4. Frequency Response of Common Emitter Amplifier.
5. Frequency Response of Common Source Amplifier.
6. Measurement of Parameters of Emitter Follower and Source Follower; R_i , A_v , A_i & R_o .
7. Cascode Amplifier.
8. Two Stage RC-Coupled Amplifier.
9. Voltage Series Feedback Amplifier.
10. Voltage Shunt Feedback Amplifier.
11. Complementary Symmetry Push-pull amplifier.
12. Class-A Power Amplifier.
13. RC Phase Shift Oscillator.
14. Colpitt's Oscillators.
15. Hartley Oscillators.

1. HALF WAVE RECTIFIER


Aim:

01. To observe the output waveform of half wave rectifier with and without filter
02. To find ripple factor and percentage regulation of FWR with & without filter

Apparatus:

Silicon Diodes BY126
 Resistance 1 k Ω
 Capacitor 470 uF CRO
 Digital Multimeter

Circuit Diagram:

 

Theory:

The half wave rectifier consists of one rectifier circuit with common load. These are connected in such a way that conduction takes place through one diode in alternate half-cycles and current through the load is sum of two currents. Thus, the output voltage waveform contains half sinusoids in the two half-cycles of the AC input signal.

The output of a rectifier is a pulsating DC consisting of a DC component and superimposed ripple. A way to eliminate or reduce the ripple to the required level is to use a filter.

PROCEDURE:**Without filter:**

01. Connect the circuit as per the circuit diagram
02. Connect CRO across the load
03. Note down the peak value V_M of the signal observed on the CRO
04. Switch the CRO into DC mode and observe the waveform. Note down the DC shift
05. Calculate V_{rms} and V_{dc} values by using the formulae

Calculate V_{rms} & V_{dc} by using the formulas

$$V_{rms} = V_M / \sqrt{2}, \quad I_{rms} = I_M / \sqrt{2}$$

$$V_{dc} = 2V_M / \pi, \quad I_{dc} = 2I_M / \pi,$$

Where V_r is the peak to peak amplitude of filter output

06. Calculate the ripple factor by using the formulae

$$\text{Ripple factor} = V_{ac} / V_{dc} = \sqrt{V_{rms}^2 - V_{dc}^2} / V_{dc}$$

07. Remove the load and measure the voltage across the circuit. Take down the value as V_{NL} ; calculate the percentage of voltage regulation using the formulae

$$\% \text{ Regulation} = (V_{NL} - V_{FL}) / V_{FL} * 100$$

With filter:

01. Connect the capacitor filter across the load in the above circuit diagram
02. Proceed with the same procedure mentioned above to measure V_r value from the CRO and also dc shift from CRO
03. Calculate V_{rms} & V_{dc} by using the formulas

$$V_r, rms = V_{dc} / 4\sqrt{3fCR_L}$$

$$V_{dc} = 2V_M / \pi$$


Where V_r is the peak to peak amplitude of filter output

04. Calculate ripple factor and % regulation by using the formulae.


$$\text{Ripple factor} = V_{rms}/V_{dc} = 1/4\sqrt{3fCR_L}$$

$$\% \text{Regulation} = (V_{NL} - V_{FL})/V_{FL} * 100$$


EXPECTED WAVE FORMS:

 

RECTIFIED OUTPUT:

 

FILTER OUTPUT

 

Precautions:

1. Wires should be checked for good continuity.
2. Carefully note down the readings with out any errors.

Result:

2. FULL WAVE RECTIFIER

Aim:

01. To observe the output waveform of full wave rectifier with and without filter
02. To find ripple factor and percentage regulation of FWR with & without filter

Apparatus:


Silicon Diodes BY126

Resistance 1 k Ω ,

Capacitor 470 μ F CRO

Digital Multimeter

Circuit Diagram:

 

Theory:

The full wave rectifier consists of two half wave rectifier circuits with common load. These are connected in such a way that conduction takes place through two diodes in alternate half-cycles and current through the load is sum of two currents. Thus, the output voltage waveform contains two half sinusoids in the two half-cycles of the AC input signal.

The output of a rectifier is a pulsating DC consisting of a DC component and superimposed ripple. A way to eliminate or reduce the ripple to the required level is to use a filter.

PROCEDURE:**Without filter:**

01. Connect the circuit as per the circuit diagram
02. Connect CRO across the load
03. Note down the peak value V_M of the signal observed on the CRO
04. Switch the CRO into DC mode and observe the waveform. Note down the DC shift
05. Calculate V_{rms} and V_{dc} values by using the formulae

Calculate V_{rms} & V_{dc} by using the formulas

$$V_{rms} = V_M / \sqrt{2}, \quad I_{rms} = I_M / \sqrt{2}$$

$$V_{dc} = 2V_M / \pi, \quad I_{dc} = 2I_M / \pi,$$

Where V_r is the peak to peak amplitude of filter output

06. Calculate the ripple factor by using the formulae

$$\text{Ripple factor} = V_{ac} / V_{dc} = \sqrt{V_{rms}^2 - V_{dc}^2} / V_{dc}$$

07. Remove the load and measure the voltage across the circuit. Take down the value as V_{NL} ; calculate the percentage of voltage regulation using the formulae

$$\% \text{ Regulation} = (V_{NL} - V_{FL}) / V_{FL} * 100$$

With filter:

01. Connect the capacitor filter across the load in the above circuit diagram
02. Proceed with the same procedure mentioned above to measure V_r value from the CRO and also dc shift from CRO
03. Calculate V_{rms} & V_{dc} by using the formulas

$$V_{r, rms} = V_{dc} / 4\sqrt{3fCR_L}$$

$$V_{dc} = 2V_M / \pi$$


Where V_r is the peak to peak amplitude of filter output

04. Calculate ripple factor and % regulation by using the formulae.


$$\text{Ripple factor} = V_{rms}/V_{dc} = 1/4\sqrt{3fCR_L}$$

$$\% \text{Regulation} = (V_{NL} - V_{FL})/V_{FL} * 100$$


EXPECTED WAVE FORMS:

 

RECTIFIED OUTPUT:

 

FILTER OUTPUT

 

Precautions:

1. Wires should be checked for good continuity.
2. Carefully note down the readings with out any errors.

Result:

3. BRIDGE RECTIFIER

Aim:

1. To observe the output waveform of bridge rectifier with and without filter
2. To find ripple factor and percentage of regulation of bridge rectifier with and without filter

Apparatus:

Silicon Diodes BY126


Resistance 1 K Ω

Capacitor 470 μ F

CRO

Multimeter

Circuit Diagram:

 

Theory:

The bridge is seen to consist of four diodes connected with their arrowhead symbols all pointing toward the positive output terminal of the circuit.

During the positive half cycle of input voltage, the load current flows from the positive input terminal through D1 to R_L and then through R_L and D4 back to the negative input terminal. During this time, the positive input terminal is applied to the cathode of D2 so it is reverse biased and similarly D3 is also reverse biased. These two diodes are forward biased during negative half cycle; D1 & D4 are reverse biased during this cycle. And finally both half cycles are rectified.

Procedure:

Without filter:

01. Connect the circuit as per the circuit diagram.
02. Connect CRO across the load
03. Note down the peak value V_M of the signal observed on the CRO
04. Switch the CRO into DC mode and observe the waveform. Note down the DC shift.
05. Calculate V_{rms} and V_{dc} values by using the formulae

$$V_{rms} = V_M / \sqrt{2}, \quad I_{rms} = I_M / \sqrt{2},$$

$$V_{dc} = 2V_M / \pi, \quad I_{dc} = 2I_M / \pi$$
06. Calculate the ripple factor by using the formulae

$$R = \sqrt{(V_{rms} / V_{dc})^2 - 1}$$
07. Remove the load and measure the voltage across the circuit take down the value as V_{NL} . Calculate the percentage of voltage regulation using the formula




$$\text{Regulation} = (V_{NL} - V_{FL}) / V_{FL} * 100$$

With Filter:

01. Connect the capacitor filter across the load in the above circuit diagram.
02. Procedure mentioned above to measure V_r value and also dc shift from CRO
03. Calculate V_{rms} by using the formula

Where V_r is the peak to peak amplitude of filter output
04. Calculate ripple factor and % regulation by using the formulae

$$\text{Regulation} = (V_{NL} - V_{FL}) / V_{FL} * 100$$

   EXPECTED WAVE FORMS:**RECTIFIED OUTPUT:****FILTER OUTPUT****Precautions:**

01. Wires should be checked for good continuity.
02. Carefully note down the readings with out any errors.

Result:

4. COMMON EMITTER AMPLIFIER

AIM: To find the voltage gain of a CE amplifier and to find its frequency response

APPARATUS:

Transistor BC107


Resistors

Capacitors

CRO

Signal generator

CIRCUIT DIAGRAM:

 

THEORY:

The CE amplifier is a small signal amplifier. This small signal amplifier accepts low voltage ac inputs and produces amplified outputs. A single stage BJT circuit may be employed as a small signal amplifier; has two cascaded stages give much more amplification.

Designing for a particular voltage gain requires the use of a ac negative feedback to
BAPATLA ENGINEERING COLLEGE (Autonomous):: BAPATLA

stabilize the gain. For good bias stability, the emitter resistor voltage drop should be much larger than the base-emitter voltage. And R_e resistor will provide the required negative feedback to the circuit. C_E is provided to provide necessary gain to the circuit. All bypass capacitors should be selected to have the smallest possible capacitance value, both to minimize the physical size of the circuit for economy. The coupling capacitors should have a negligible effect on the frequency response of the circuit.

PROCEDURE:


1. Connect the circuit as per the circuit diagram.
2. Give 100Hz signal and 20mv p-p as V_s from the signal generator
3. Observe the output on CRO and note down the output voltage.
4. Keeping input voltage constant and by varying the frequency in steps 100Hz-1MHz, note down the corresponding output voltages.
5. Calculate gain in dB and plot the frequency response on semi log sheet

TABULAR FORM:

Input voltage (V_i)=

.NO	FREQUENCY	OUTPUT VOLTAGE(V_o)	GAIN $A_v=V_o/V_i$	GAIN IN dB 20 log gain

MODEL GRAPH:

 

- Precautions:**
01. Wires should be checked for good continuity.
 02. Transistor terminals must be identified and connected carefully.

Result:

5. COMMON SOURCE AMPLIFIER

AIM:

To find the voltage gain of a CS amplifier and to find its frequency response

APPARATUS:


FETBFW10

RESISTORS

Capacitors

Signal generator &CRO

CIRCUIT DIAGRAM:

 

THEORY:

The CS amplifier is a small signal amplifier. For good bias stability, the source resistor voltage drop should be as large as possible. Where the supply voltage is small, V_s may be reduced to a minimum to allow for the minimum level of V_{ds} . R_2 is usually selected as $1M\Omega$ or less as for BJT capacitor coupled circuit, coupling and bypass capacitors should be selected to have the smallest possible capacitance values. The largest capacitor in the circuit sets the circuit low 3dB frequency (capacitor C_2). Generally to have high input impedance FET is used. As in BJT circuit R_L is usually much larger than Z_o and Z_i is often much larger than R_s .

PROCEDURE:

1. Connect the circuit as per the circuit diagram
2. Give 1 KHz signal and 25 mv (P-P) as V_s from signal generator.
3. Observe the output on CRO for proper working of the amplifier.
4. After ensuring the amplifier function, vary signal frequency from 50 Hz to 600 Hz in proper steps for 15-20 readings keeping $V_s = 25\text{mv(P-P)}$ at every frequency ,note down the resulting output voltage and tabulate in a table
5. Calculate gain in dB and plot on semi log graph paper for frequency Vs gain


in dB

TABULAR FORM:

Input voltage =

S.NO	FREQUENCY	OUTPUT VOLTAGE(V_o)	GAIN $A_v = V_o/V_i$	GAIN IN dB 20 log gain

MODEL GRAPH:

 

- PRECAUTIONS:**
1. Wires should be checked for good continuity
 - 2 FET terminals must be identified and connected carefully.

RESULT:


6. MEASUREMENT OF PARAMETERS OF EMITTER FOLLOWER AND SOURCE FOLLOWER

Aim: To calculate the Voltage gain, Current gain, input resistance and output resistance of Emitter follower & source follower.

Apparatus:

FETBFW10
 Transistor BC107
 Resistors
 Capacitors
 CRO
 Function Generator.
 Multi meter

CIRCUIT DIAGRAM:

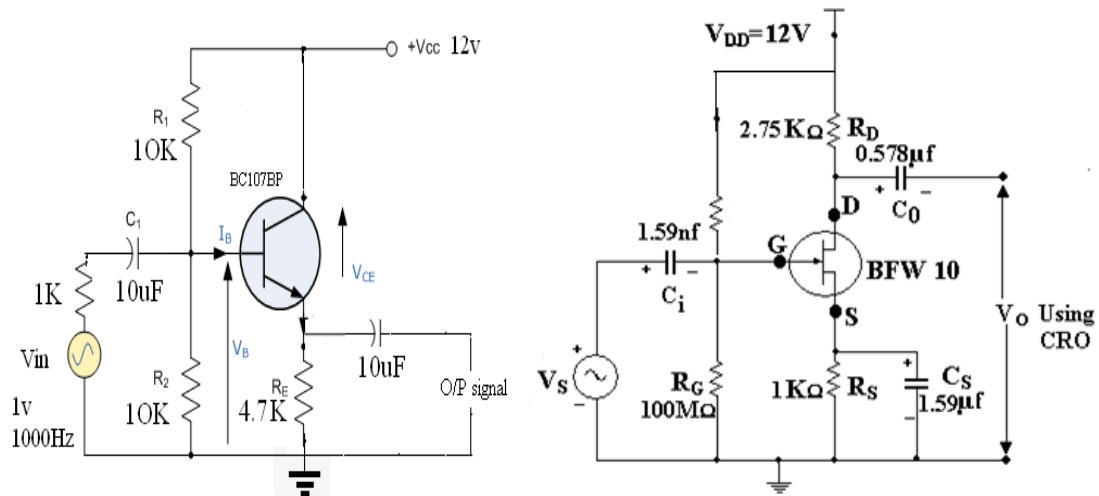

THEORY: EMITTER FOLLOWER

The common collector circuit is also known as emitter follower. The ac output voltage from a CC circuit is essentially the same as the input voltage; there is no voltage gain or phase shift. Thus, the CC circuit can be said to have a voltage gain of 1. The fact that the CC output voltage follows the changes in signal voltage gives the circuit its other name emitter follower. The input impedance of a CC amplifier is high. Output impedance is low and the

Voltage gain is almost unity. Because of these Characteristics the CC circuit is normally used as a buffer amplifier, placed between a high impedance signal source and a low impedance load

SOURCE FOLLOWER

The FET common drain circuit has the output voltage developed across the source resistor R_s . Here the ac output voltage is closely equal to the ac input voltage, and the circuit can be said to have unity gain. Because the output voltage at the source terminal follows the signal voltage at the gate, the common drain circuit is also known as a source follower.

A common drain circuit has a voltage gain approximately equal to 1, no phase shift between input and output, very high input impedance and low output impedance. Because of its high Z_i , low Z_o and unity gain the CD circuit is used as a buffer amplifier between a high impedance signal source and a low impedance load.

PROCEDURE:

1. Connect the circuit as per the circuit diagram.
2. Apply V_{slv} 1 KHz signal from the signal generator.
3. Observe corresponding output from the CRO and then calculate voltage gain using the formula $A_v = V_o/V_i$.
4. Measure voltage across AB terminals and then calculate input current by using the formula $I_{in} = V_{ab}/R_{ab}$.
5. Measure current flowing through resistor at Source (or Emitter) terminal and note down it as I_{out} .
6. Calculate Current gain using the formula $A_I = I_{in}/I_{out}$.
7. Calculate input resistance using the formula $R_{in} = V_{in}/I_{in}$.
8. To calculate the output resistance, connect the pot at the output and vary the resistance of the pot up to half of the output with R_L is equal to infinity. The resistance of pot is the output resistance.

PRECAUTIONS:

1. Wires should be checked for good continuity
2. FET terminals must be identified and connected carefully.

RESULT:

7. CASCODE AMPLIFIER


AIM:

To measure voltage gain, input resistance and output resistance of cascade Amplifier.

APPARATUS:

Transistor BC107
Resistors
Signal generator
Capacitors

CIRCUIT DIAGRAM:

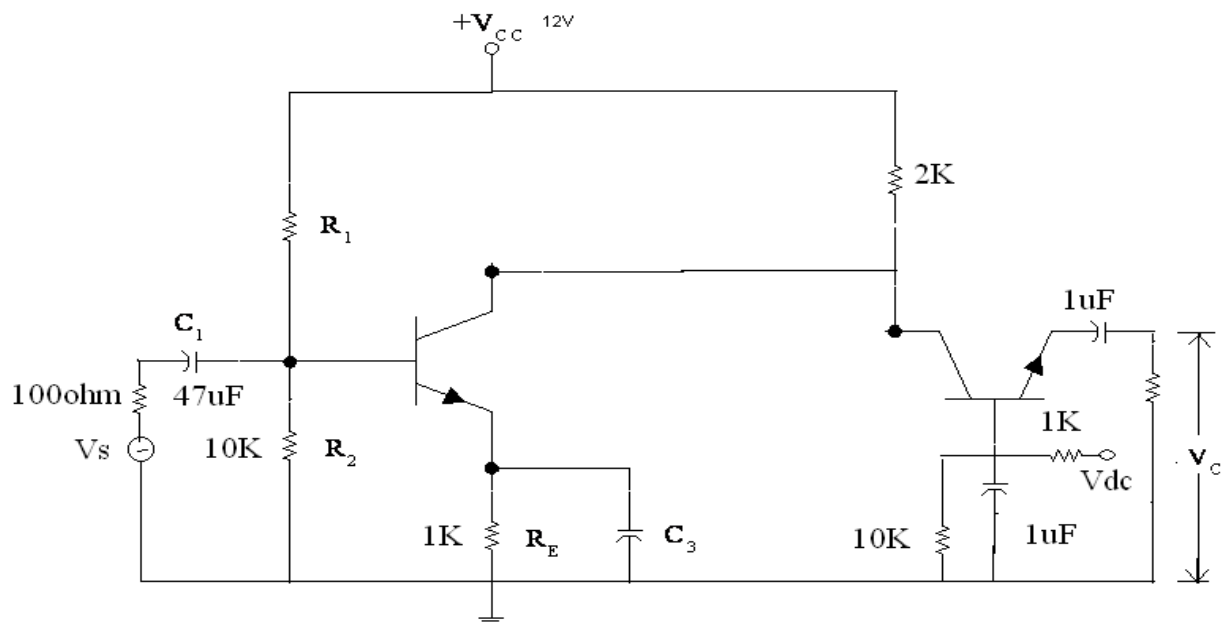

THEORY:

Cascode amplifier is a cascade connection of a common emitter and common base amplifiers. It is used for amplifying the input signals. The common application of cascode amplifier is for impedance matching. The low impedance of CE stage is matched with the medium of the CB stage.

DESIGN:

$$I_{B1} = (V_{CE} - V_{BE}) / R_{B1}$$

$$I_{C1} = I_{E2} = I_{C2} = \beta I_{B1}$$

$$V_{C1} = V_{E2} = V_{B2} - V_{BE}$$

$$V_{C2} = V_{CC} - I_{C2} * R_{C2}$$

$$V_{CE2} = V_{C2} - V_{E2}$$

$$R_{in} = R_{B1} \parallel \beta_1 R_{E1}$$

$$A_{V1} = -R_{L1} / R_{E1} = -1$$

$$R_O = R_{C2}$$

$$R_{L2} = R_{C2} \parallel R_L$$

$$A_{V2} = R_{L2} / R_{E2}$$

$$A_V = A_{V1} * A_{V2}$$

PRECAUTIONS:

1. Wires should be checked for good continuity
2. Take the readings carefully

RESULT:

8. TWO STAGE RCCOUPLED AMPLIFIERS

AIM:

To obtain the frequency response of a two stage RC coupled amplifier.

Apparatus:

Transistors


BC 107

Resistors

Capacitors

Signal Generators & CRO

Circuit Diagram:

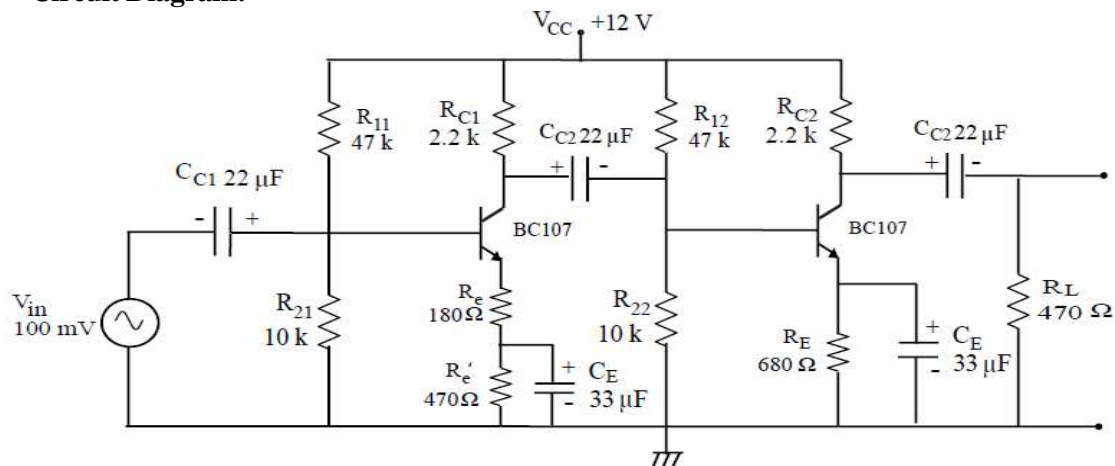

Theory :

The output from a single stage amplifier is usually insufficient to drive an o/p device. To achieve more gain, the o/p of one stage is given as the input to the other stage which forms multistage amplifier. If the two stages are coupled by R and C, then the amplifier is called RC coupled amplifier. The performance of an amplifier can be determined from the following terms.

Gain:-

The gain is defined as ratio of output to input. The gain of multistage amplifier is equal to the product of gains of individual stages i.e $G=G_1.G_2.G_3$.

Frequency Response:-

At low frequencies (<50HZ) the reactance of coupling capacitor C_c is high and hence very small part of signal will pass from one stage to next stage. This increases the loading effect of next stage and reduces the voltage gain.


At high frequencies, capacitance reduces. Due to this base emitter junction is low which increases the base current. This reduces the amplification factor.

At mid frequencies, the voltage gain of the amplifier is constant. In this range, as frequency increases, reactance of C_C reduces which tends to increase the gain. At the same time, lower reactance means higher reactance of first stage and hence lower gain, these two factors cancel each other resulting in a uniform gain at mid frequency.

PROCEDURE

01. Connect the circuit as per the circuit diagram
02. Give 1 KHz signal, 25 mV (p-p) as V_s from signal generator
03. Observe the output on CRO for proper working of the amplifier
04. After ensuring the amplifier function, vary signal frequency from 50 Hz to 600 Hz in proper steps for 15 to 20 readings. Keeping $V_s = 25$ mV (p-p) at every frequency, note down the resetting output voltage and tabulate in a table.
05. Calculate gain db and plot on semi log graph paper for frequency VS gain db.

Expected waveforms:

 

Tabular Form:

S.NO	FREQUENCY (HZ)	OUTPUT VOLTAGE(GAIN $A_v=V_o/V_i$	GAIN IN dB

RESULT:

9. VOLTAGE SERIES FEEDBACK AMPLIFIER


Aim:

To plot the frequency response characteristics of voltage series feed back amplifier.

Apparatus Required:

Transistor
Resistors and capacitors,
Function generator,
CRO

Circuit Diagram:

 

THEORY:

When any increase in the output signal results into the input in such a way as to cause the decrease in the output signal, the amplifier is said to have negative feedback.

The advantages of providing negative feedback are that the transfer gain of the amplifier with feedback can be stabilized against variations in the hybrid parameters of the transistor or the parameters of the other active devices used in the circuit. The most advantage of the negative feedback is that by proper use of this, there is significant improvement in the frequency response and in the linearity of the operation of the amplifier. This disadvantage of the negative feedback is that the voltage gain is decreased.

In Current-Series Feedback, the input impedance and the output impedance are increased. Noise and distortions are reduced considerably.

PROCEDURE:

1. Connections are made as per circuit diagram.
2. Keep the input voltage constant at 20mV peak-peak and 1kHz frequency. For different values of load resistance, note down the output voltage and calculate the gain by using the expression

$$A_v = 20\log(V_0 / V_i) \text{ dB}$$

3. Remove the emitter bypass capacitor and repeat STEP 2. And observe the effect of feedback on the gain of the amplifier.
4. For plotting the frequency the input voltage is kept constant at 20mV peak-peak and the frequency is varied from 100Hz to 1MHz.
5. Note down the value of output voltage for each frequency. All the readings are tabulated and the voltage gain in dB is calculated by using expression $A_v = 20\log(V_0 / V_i) \text{ dB}$
6. A graph is drawn by taking frequency on X-axis and gain on Y-axis on semi log graph
7. The Bandwidth of the amplifier is calculated from the graph using the expression $\text{Bandwidth B.W} = f_2 - f_1$.


Where f_1 is lower cutt off frequency of CE amplifier

f_2 is upper cutt off frequency of CE amplifier

8. The gain-bandwidth product of the amplifier is calculated by using the expression

$$\text{Gain-Bandwidth Product} = 3\text{-dB midband gain} \times \text{Bandwidth.}$$

Model Graph:

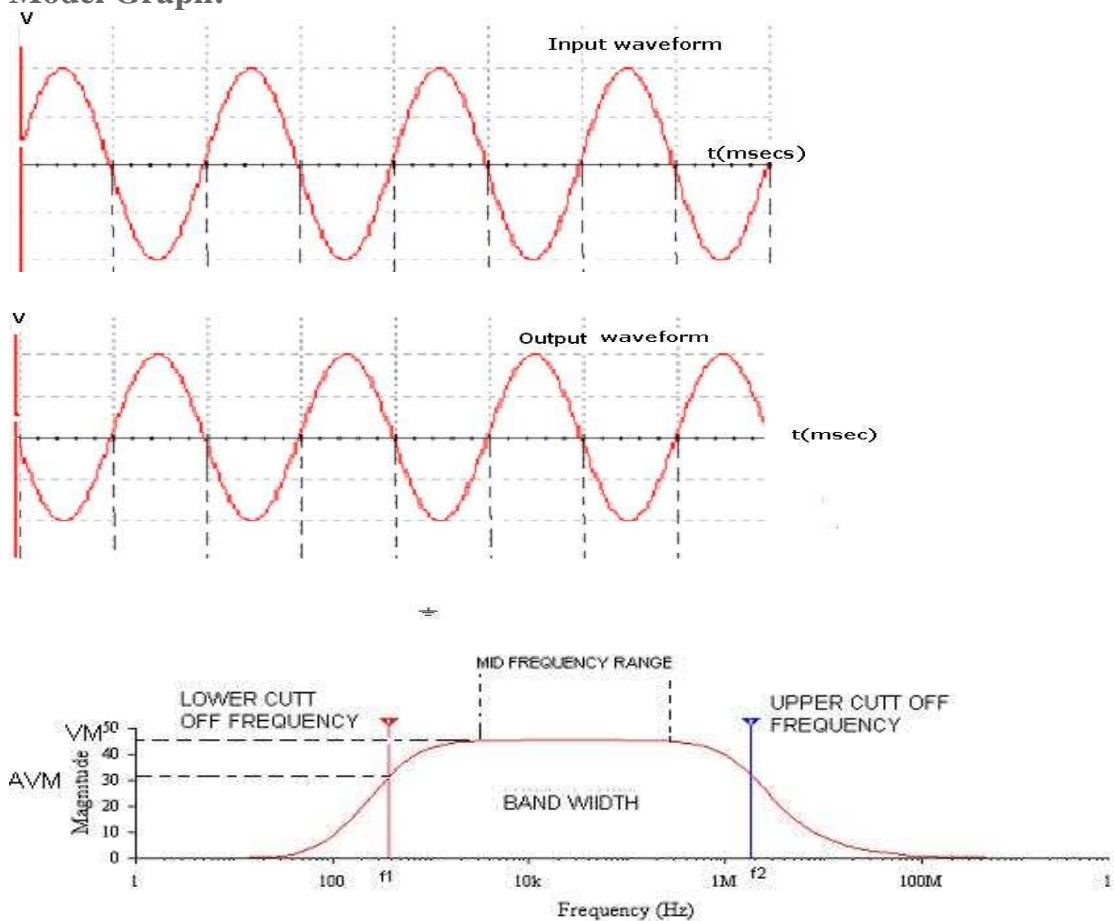

Tabular Columns:

Voltage Gain: $V_i = 20 \text{ mV}$

S.NO	Output Voltage (V _o) with feedback	Output Voltage (V _o) without feedback	Gain(dB) with feedback	Gain(dB) without feedback

PRECAUTIONS:

1. While taking the observations for the frequency response , the input voltage must be maintained constant at 20mV.
2. The frequency should be slowly increased in steps.
3. The three terminals of the transistor should be carefully identified.
4. All the connections should be correct.

RESULT:

10. Voltage Shunt Feedback Amplifier

AIM:

To measure the voltage gain of current - series feed back amplifier.

APPARATUS:

Transistor BC 107

Breadboard


Regulated Power Supply (0-30V,1A)

Function Generator

CRO(30 Mhz,dualtrace)

Resistors and Capacitors

CIRCUIT DIAGRAM:

 


THEORY:

When any increase in the output signal results into the input in such a way as to cause the decrease in the output signal, the amplifier is said to have negative feedback. The advantages of providing negative feedback are that the transfer gain of the amplifier with feedback can be stabilised against variations in the hybrid parameters of the transistor or the parameters of the other active devices used in the circuit. The most advantage of the

negative feedback is that by proper use of this, there is significant improvement in the frequency response and in the linearity of the operation of the amplifier. This disadvantage of the negative feedback is that the voltage gain is decreased.

Model Wave forms and Frequency Response:

 

PROCEDURE:

1. Connections are made as per circuit diagram.
2. Keep the input voltage constant at 20mV peak-peak and 1kHz frequency. For different values of load resistance, note down the output voltage and calculate the gain by using the expression

$$A_v = 20 \log(V_0 / V_i) \text{ dB}$$

3. Remove the emitter bypass capacitor and repeat STEP 2. And observe the effect of feedback on the gain of the amplifier.

4. For plotting the frequency the input voltage is kept constant at 20mV peak-peak and the frequency is varied from 100Hz to 1MHz.
5. Note down the value of output voltage for each frequency. All the readings are tabulated and the voltage gain in dB is calculated by using expression $A_v = 20\log (V_o / V_i)$ dB
6. A graph is drawn by taking frequency on X-axis and gain on Y-axis on semi log graph sheet
7. The Bandwidth of the amplifier is calculated from the graph using the expression Bandwidth B.W = $f_2 - f_1$.
Where f_1 is lower cutt off frequency of CE amplifier
 f_2 is upper cutt off frequency of CE amplifier
8. The gain-bandwidth product of the amplifier is calculated by using the expression Gain-Bandwidth Product = 3-dB midband gain X Bandwidth.

Tabular Columns:

Voltage Gain: $V_i = 20$ mV

S.NO	Output Voltage (V _o) with feedback	Output Voltage (V _o) without feedback	Gain(dB) with feedback	Gain(dB) without feedback

PRECAUTIONS:

1. While taking the observations for the frequency response , the input voltage must be maintained constant at 20mV.
2. The frequency should be slowly increased in steps.
3. The three terminals of the transistor should be carefully identified.
4. All the connections should be correct.

RESULT:

11. Complementary Symmetry Push-pull amplifier.


AIM:

To construct a Class B complementary symmetry power amplifier and observe the waveforms with and without cross-over distortion and to compute maximum output power and efficiency.

APPARATUS REQUIRED:

S.No.	Name	Range	Quantity
1.	Transistor	CL100, BC558	1,1
2.	Resistor	4.7k Ω , 15k Ω	2,1
3.	Capacitor	100 μ F	2
4.	Diode	IN4007	2
5.	Signal Generator	(0-3)MHz	1
6.	CRO	30MHz	1
7.	Regulated power supply	(0-30)V	1
8.	Bread Board		1

CIRCUIT DIAGRAM

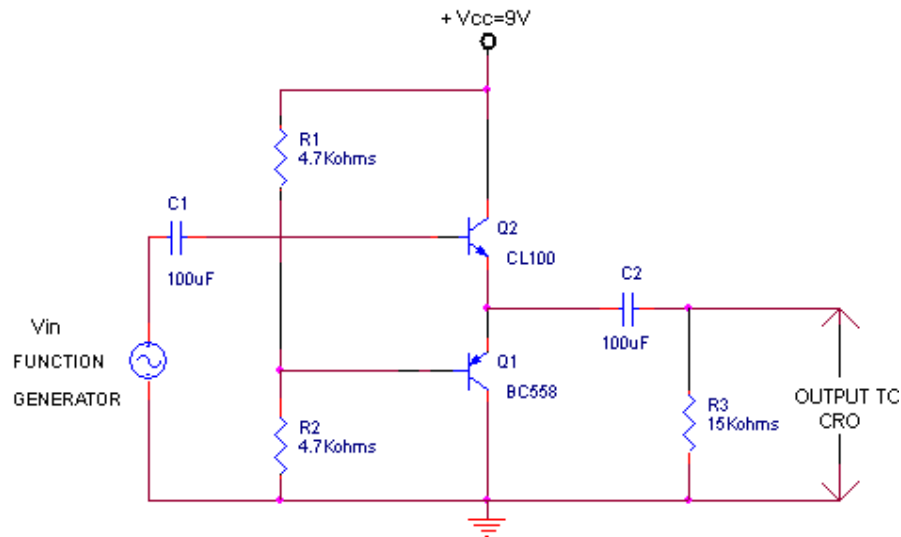

FORMULA:

Input power, $P_{in} = 2V_{cc}I_m / \pi$

Output power, $P_{out} = V_m I_m / 2$

Power Gain or efficiency, $\eta = \pi/4 (V_m / V_{cc}) \times 100$

THEORY:

A power amplifier is said to be Class B amplifier if the Q-point and the input signal are selected such that the output signal is obtained only for one half cycle for a full input cycle. The Q-point is selected on the X-axis. Hence, the transistor remains in the active region only for the positive half of the input signal.

There are two types of Class B power amplifiers: Push Pull amplifier and complementary symmetry amplifier. In the complementary symmetry amplifier, one n-p-n and another p-n-p transistor is used. The matched pair of transistor are used in the common collector configuration. In the positive half cycle of the input signal, the n-p-n transistor is driven into active region and starts conducting and in negative half cycle, the p-n-p transistor is driven into conduction. However there is a period between the crossing of the half cycles of the input signals, for which none of the transistor is active and output, is zero

OBSERVATION

OUTPUT SIGNAL

AMPLITUDE :

TIME PERIOD :


CALCULATION

POWER, $P_{IN} = 2V_{CC} I_m / \pi$



OUTPUT POWER, $P_{OUT} = V_m I_m / 2$

EFFICIENCY, $\eta = (\pi/4) (V_m / V_{CC}) \times 100$

MODEL GRAPH

 

INPUT SIGNAL

  OUTPUT SIGNAL
WITHOUT DIODE**PROCEDURE:**

1. Connections are given as per the circuit diagram without diodes.
2. Observe the waveforms and note the amplitude and time period of the input signal and distorted waveforms.
3. Connections are made with diodes.
4. Observe the waveforms and note the amplitude and time period of the input signal and output signal.
5. Draw the waveforms for the readings.
6. Calculate the maximum output power and efficiency.

Hence the nature of the output signal gets distorted and no longer remains the same as the input. This distortion is called cross-over distortion. Due to this distortion, each transistor conducts for less than half cycle rather than the complete half cycle. To overcome this distortion, we add 2 diodes to provide a fixed bias and eliminate cross-over distortion.

RESULT:

12. Class-A Power Amplifier.


AIM:

To construct a Class A power amplifier and observe the waveform and to compute maximum output power and efficiency.

APPARATUS REQUIRED:

S.No.	Name	Range	Quantity
1.	Transistor	CL100, BC558	1,1
2.	Resistor	47k Ω ,33 Ω ,220 Ω ,	2,1
3.	Capacitor	47 μ F	2
4.	Signal Generator	(0-3)MHz	1
5.	CRO	30MHz	1
6.	Regulated power supply	(0-30)V	1
7.	Bread Board		1

CIRCUIT DIAGRAM

 

THEORY:

The power amplifier is said to be Class A amplifier if the Q point and the input signal are selected such that the output signal is obtained for a full input signal cycle.

For all values of input signal, the transistor remains in the active region and never enters into cut-off or saturation region. When an a.c signal is applied, the collector voltage varies sinusoidally hence the collector current also varies sinusoidally. The collector current flows for 360° (full cycle) of the input signal. i.e the angle of the collector current flow is 360° .

PROCEDURE:

1. Connect the circuit as per the circuit diagram.
2. Set $V_i = 50$ mv, using the signal generator.
3. Keeping the input voltage constant, vary the frequency from 10 Hz to 1M Hz in regular steps and note down the corresponding output voltage.
4. Plot the graph; Gain (dB) vs Frequency(Hz).

FORMULA

$$\text{Maximum power transfer} = P_{o,\max} = V_o^2 / R_L$$

$$\text{Effeciency, } \eta = P_{o,\max} / P_c$$

TABLES:

Keep the input voltage constant, $V_{in} =$

Frequency (in Hz)	Output Voltage (in volts)	Gain= $20 \log(V_o/V_{in})$ (in dB)

RESULT:

13. RC Phase Shift Oscillator.


Aim:

To design and set up an RC phase shift oscillator using BJT and to observe the sinusoidal output waveform.

Equipments required:

Transistor,
dc source,
capacitors, resis-tors,
potentiometer,
breadboard and CRO.

Circuit Diagram:

 

Theory:

An oscillator is an electronic circuit for generating an ac signal voltage with a dc supply as the only input requirement. The frequency of the generated signal is decided by the circuit elements. An oscillator requires an amplifier, a frequency selective network, and a positive feedback from the output to the input. The Barkhausen criterion for sustained oscillation is $A_{\beta} = 1$ where A is the gain of the amplifier and β is the feedback factor. The unity gain means signal is in phase. (If the signal is 180° out of phase, gain will be 1.). If a common emitter amplifier is used, with a resistive collector load, there is a 180° phase shift between the voltages at the base and the collector.


In the figure shown, three sections of phase shift networks are used so that each section introduces approximately 60° phase shift at resonant frequency. By analysis, resonant frequency f can be expressed by the equation,

$$f = \frac{1}{2\pi RC \sqrt{6 + 4R_c/R}}$$

Procedure:

1. Connections are made as per circuit diagram.
2. Connect CRO output terminals and observe the waveform.
3. Calculate practically the frequency of oscillations by using the expression $f = 1 / T$ ($T =$ Time period of the waveform)
4. Repeat the above steps 2,3 for different values of L , and note down the practically values of oscillations of the RC-phase shift oscillator.
5. Compare the values of oscillations both theoretically and practically.

MODELWAVEFORM:

 

RESULT:

14. Colpitt's Oscillators

AIM: To study and calculate frequency of oscillations of colpitt's oscillator.

APPARATUS: Transistor BC 107

Capacitors 0.1 μ F - 2Nos

10 μ F - 2Nos

47 μ F - 1No

Resistors 6.8k Ω , 1k Ω , 100k Ω

Decade Inductance Box (DIB)


Decade Resistance Box (DRB)

Cathode Ray Oscilloscope (CRO)

Regulated Power Supply (0-30V)

Connecting Wires

CIRCUITDIAGRAM:

 

THEORY:

The tank circuit is made up of L_1 , C_4 and C_5 . The resistance R_2 and R_3 provides the necessary biasing. The capacitance C_2 blocks the D.C component. The frequency of oscillations is determined by the values of L_1 , C_4 and C_5 , and is given by

$$f = 1 / (2\pi (C_T L_1)^{1/2}) \text{ Where } C_T = C_1 C_2 / (C_1 + C_2)$$

The energy supplied to the tank circuit is of correct phase. The tank circuit provides 180° out of phase. Also the transistor provides another 180° . In this way, energy feedback to the tank circuit is in phase with the generated oscillations.

PROCEDURE:


1. connections are made as per circuit diagram.
2. Connect CRO output terminals and observe the waveform.
3. Calculate practically the frequency of oscillations by using the expression

$$f = 1 / T \text{ (T= Time period of the waveform)}$$
4. Repeat the above steps 2,3 for different values of L, and note down the practical values of oscillations of the collpitt’s oscillator.
5. Compare the values of oscillations both theoretically and practically.

OBSERVATIONS:

Inductance (mH)	Theoretical Frequency (Hz)	Practical Frequency (Hz)

MODELWAVEFORM:

 

PRECAUTIONS:

1. All the connections should be correct.
2. Transistor terminals must be identified properly.
3. Reading should be taken without any parallax error.

RESULT:

15. Hartley Oscillators


AIM:

To study and calculate frequency of oscillations of Hartley oscillator. Compare the frequency of oscillations, theoretically and practically.

APPARATUS:

- Transistor BC 107
- Capacitors 0.1 μ F, 10 μ F
- Resistors 6.8Kohm, 1Kohm and 100Kohm
- Decade inductance box (DIB)
- Decade resistance box (DRB)
- Cathode ray oscilloscope
- Bread board
- Regulated power supply (0-30V)
- Connecting wires

CIRCUIT DIAGRAM:

 

THEORY:

Hartley oscillator is very popular and is commonly used as a local oscillator in radio receivers. It has two main advantages viz... Adaptability to wide range of frequencies and easy to tune. The tank circuit is made up of L1, L2, and C1. The coil L1 is inductively coupled to coil L2, the combination functions as auto transformer. The resistances R2 and R3 provide the necessary biasing. The capacitance C2 blocks the d.c component. The frequency of oscillations is determined by the values of L1, L2 and C1 and is given by,

$$F=1/(2\pi(C1(\sqrt{L1+L2})))$$

The energy supplied to the tank circuit is of correct phase. The auto transformer provides 180° out of phase. Also another 180° is produced

By the transistor. In this way, energy feedback to the tank circuit is in phase with the generated oscillations.

PROCEDURE:


1. Connections are made as per the circuit diagram.
2. Connect CRO at output terminals and observe wave form.
3. Calculate practically the frequency of oscillations by using the Expression.

$$F=1/T, \text{ Where } T= \text{Time period of the waveform}$$

4. Repeat the above steps 2, 3 for different values of L1 and note Down practical values of oscillations of colpitts oscillator.
5. Compare the values of frequency of oscillations both theoretically And Practically.

OBSERVATIONS:

CAPACITANCE(μF)	Theoretical frequency (KHZ)	Practical frequency (KHZ)

 MODELWAVEFORM:**PRECAUTIONS:**

1. All the connections should be correct.
2. Transistor terminals must be identified properly.
3. Reading should be taken without any parallax error.

RESULT: