

Hall Ticket Number:

--	--	--	--	--	--	--	--	--

IV/IV B.Tech DEGREE EXAMINATION**OCTOBER, 2016****Electronics and Communication Engineering****Sixth Semester****Linear Integrated circuits & Applications****Time:** Three Hours**Maximum :** 60 Marks*Answer Question No.1 compulsorily.*

(1X12 = 12 Marks)

Answer ONE question from each unit.

(4X12=48 Marks)

1. Answer all questions

(12X1=12 Marks)

- a) Define i/p offset voltage.
- b) What are the ideal characteristics of an op-amp?
- c) What is precision rectifier?
- d) Define Slew rate of an op-amp.
- e) What is frequency stability?
- f) What are the limitations of comparator?
- g) What is V_O for a 4bit DAC whose V_R is 10V and the i/p binary number is 0101?
- h) Define Hysteresis.
- i) What is clamping?
- j) Define percentage resolution.
- k) What is capture range of PLL?
- l) Draw the circuit diagram of All pass filter.

UNIT – I

2.a Explain about voltage series feedback amplifier. (6M)

2.b Consider the lossy integrator if $R_1=20k$, $R_F=200k$, $C_F=10nF$, determine the lower frequency limit of Integration, also sketch o/p wave form for an i/p of 1V peak sine wave at 5 kHz.

(6M)

(OR)

3.a Explain the ac characteristics of an op-amp. (6M)

3.b Explain differential instrumentation amplifier with a neat diagram. (6M)

UNIT – II4.a Derive f_{osc} & A_v for a RC phase shift oscillator using an op-amp and also design the oscillator to Oscillate at 500Hz. (8M)

4.b Explain about Voltage controlled oscillator with a neat sketch. (4M)

(OR)

5.a Explain the operation of a triangular wave generator also derive the frequency of oscillations of the triangular wave generator. (6M)

5.b Explain about Schmitt trigger. Find V_H if $R_1=100\Omega$, $R_2=56\Omega$ & supply voltage $\pm 15v$. (4+2=6M)

UNIT – III

- 6.a Explain the types of clippers with necessary waveforms. (6M)
6.b Draw the circuit of R-2R 2 bit DAC and derive expression for analog o/p. (6M)

(OR)

- 7.a Give the Schematic circuit diagram of successive approximation type ADC and explain the operation with the given digital representation 11010100. (8M)
7.b Explain about Absolute value output circuit. (4M)

UNIT – IV

- 8.a Explain the operation of Astable multivibrator using 555 timer. Obtain the expression for duty cycle. (6M)
8.b Explain about 723 general purpose voltage regulator. (6M)

(OR)

- 9.a With the aid of circuit diagram explain & derive the transfer function of second order High pass filter. (6M)
9.b Design a wide band pass filter having $f_L=400\text{Hz}$, $f_H=2\text{kHz}$ & pass band gain of 4. Find the value of Q of the filter. (6M)

