

Hall Ticket Number:

--	--	--	--	--	--	--	--	--

II/IV B.Tech (Regular) DEGREE EXAMINATION

MODEL PAPER

(First Semester)

CIRCUIT THEORY

(ECE BRANCH)

Time: Three Hours

Maximum : 60 Marks

Answer Question No.1 compulsorily.

(1X12 = 12 Marks)

Answer ONE question from each unit.

(4X12=48 Marks)

(12X1=12 Marks)

1. Discuss the following

1. a) Give the KCL in word form?
- b) State Reciprocity theorem.
- c) What are Passive and Active elements?
- d) What is the difference between Mesh & Loop?
- e) Define Form factor.
- f) What are the differences between Admittance and Susceptance?
- g) Define Bandwidth.
- h) Give the formula for selectivity.
- i) What is Initial value theorem?
- j) Define Reactance power.
- k) Draw the phasor diagram of RL circuit.
- l) Define Resonance in Parallel RLC Circuit?

UNIT-I

2. a) Determine the node voltages using nodal analysis in the circuit of Fig.1
- b) Write the mesh equations for the circuit shown in Fig. 2. Next determine the values of i_1 , i_2 , i_3 .

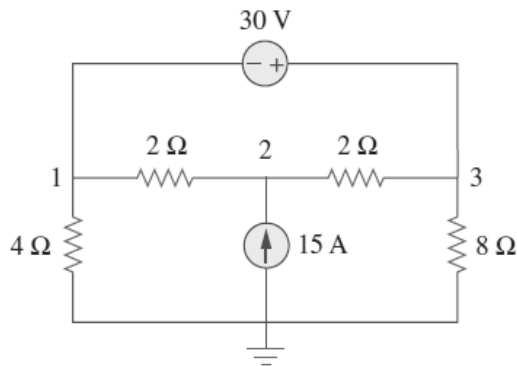


Fig.1

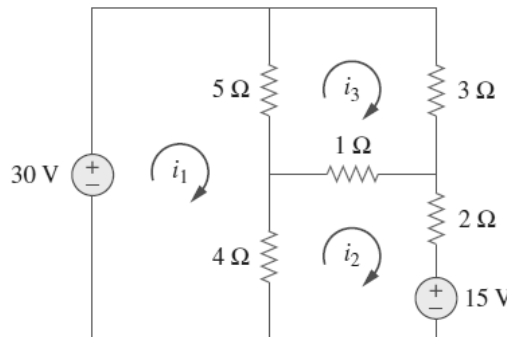


Fig.2

(OR)

3. a) Calculate v_o and I_o in the circuit of fig. 3.

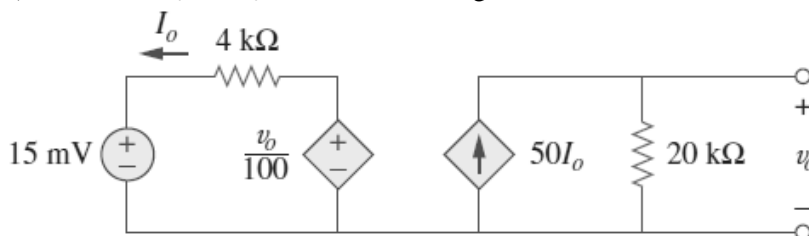


Fig. 3

- b) For the network shown in Fig. 4 develop a oriented graph and construct the cut set matrix.

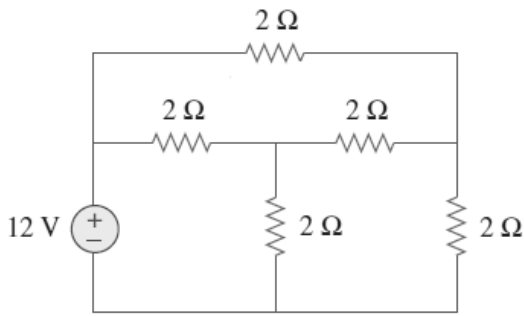


Fig. 4

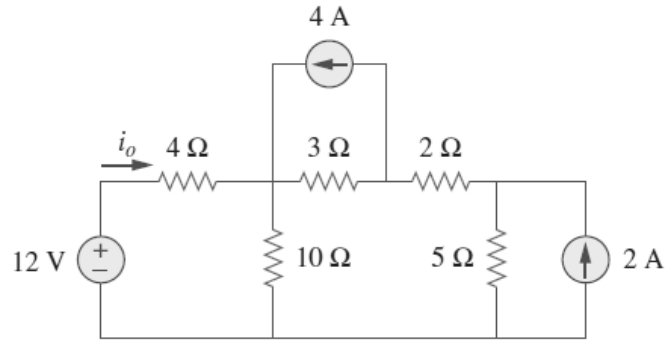


Fig. 5

UNIT-II

4. a) Use superposition theorem to obtain i_o for the circuit in Fig. 5
b) State and prove Millman's theorem.

OR

5. a) State and prove maximum power transfer theorem and Illustrate with an example.
b) Apply thevenin's theorem to find V_o in the circuit in Fig. 6

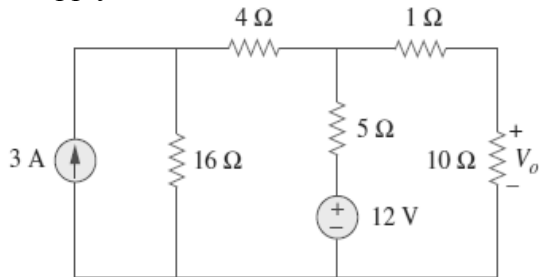


Fig. 6

UNIT-III

6.a) A series RLC circuit with $R=5$ ohms, $L=1$ henries and $C=0.5$ farads has a constant voltage of 5 Volts applied at time $t=0$. Determine the transient current $i(t)$. Assume zero initial conditions.

b) A series RC circuit with $R = 100$ ohms and $C = 25$ F and a sinusoidal voltage of $150\sin(500t)$ Volts are applied. Find the expression for total current.

OR

7. a) Find the average power absorbed by the 10 ohm resistor for the circuit in Fig. 7


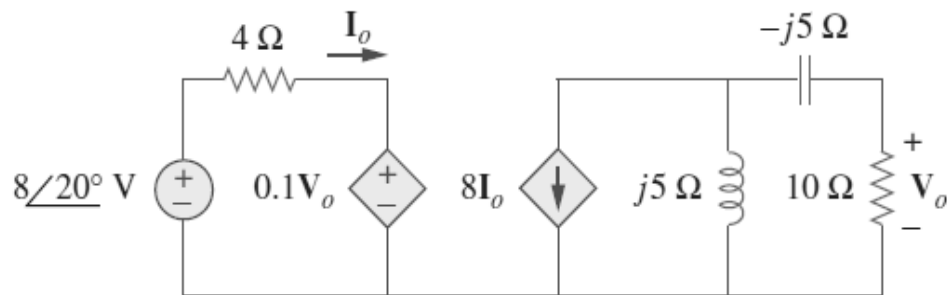


Fig. 7

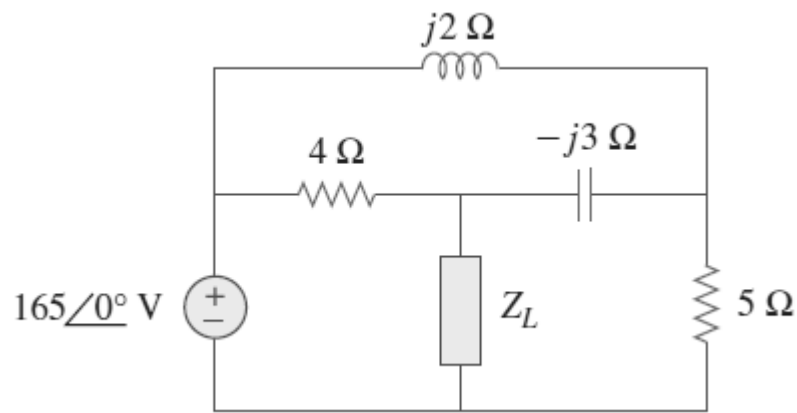- b) Find the value of Z_L which will absorb maximum average power and also maximum value of the power for the circuit shown



UNIT-IV

8. a) For a parallel RLC circuit, find the under damped response for $R = 10.5$ ohms, $L = 7$ Henries and $C = 1/42$ Farads.
- b) The voltage $v_s = 100 \cos \omega t$ mV is applied to a series resonant circuit composed of a 10 ohms resistance, a $200 \mu\text{F}$ capacitance, and a 2mH inductance. Use both exact and appropriate methods to calculate the current amplitude if $\omega = 48 \text{krad/s}$

OR

9. a) Find the inverse Laplace transform of $2/(s^3 + 12s^2 + 36s)$
- b) State and prove initial and final value theorems.