

Hall Ticket Number:

|  |  |  |  |  |  |  |  |  |  |
|--|--|--|--|--|--|--|--|--|--|
|  |  |  |  |  |  |  |  |  |  |
|--|--|--|--|--|--|--|--|--|--|

II/IV B.Tech (Regular) DEGREE EXAMINATION

November, 2019

Third Semester

Time: Three Hours

Electronics &amp; Instrumentation Engg.

Electronic Devices &amp; Circuits

Maximum : 50 Marks

Answer Question No.1 compulsorily.

(1X10 = 10 Marks)

Answer ONE question from each unit.

(4X10=40 Marks)

(1X10=10 Marks)

1 Answer all questions

- What is doping?
- What is drift current?
- Write law of mass action.
- Find the factor by which the reverse saturation current of silicon diode will get multiplied when the temperature is increased from  $27^{\circ}\text{C}$  to  $47^{\circ}\text{C}$ .
- Which configuration of BJT has high input resistance?
- In a BJT, write the relation between  $\alpha$  and  $\beta$ .
- Define threshold voltage of a MOSFET.
- What is the relation between  $\mu$ ,  $g_m$  and  $r_d$  in a MOSFET.
- What is the approximate voltage gain of source degenerated amplifier?
- What is the advantage of using active load in an amplifier?

## UNIT I

- Derive the expressions for intrinsic carrier concentrations using energy band model. 5M
- If the effective mass of an electron is equal to twice the effective mass of a hole, find the distance ( in electron volts ) of the Fermi level in an intrinsic semiconductor from the centre of the forbidden band at room temperature. 5M

(OR)

- List basic equations that are useful for semiconductor device analysis and describe the variables. 5M
- In a semiconductor, it is observed that three quarters of current is carried by electrons and one quarter by holes. If at this temperature, the drift speed of electrons is three times that of the holes, determine the ratio of electrons to holes in the semiconductor. 5M

## UNIT II

- Explain avalanche breakdown mechanism in a diode? 5M
- The diode current is 0.6mA when the applied voltage is 400mV and 20mA when the applied voltage is 500mV. Determine  $\eta$  at room temperature. 5M

(OR)

- Compare the three configurations of a Bipolar Junction Transistor 5M
- Determine the quiescent currents and the collector to emitter voltage for a silicon transistor with  $\beta = 50$  in the self biasing arrangement. The circuit component values are  $V_{CC} = 20\text{V}$ ,  $R_C = 2\text{K}$ ,  $R_E = 0.1\text{K}$ ,  $R_1 = 100\text{K}$  and  $R_2 = 5\text{K}$ . 5M

## UNIT III

- Explain the operation of n-channel MOSFET with neat diagrams. 5M
- Calculate the drain current of an nMOS transistor for  $V_{GS} = 0\text{V}$ ,  $1\text{V}$  and  $2\text{V}$  with device parameters as  $W = 5\mu\text{m}$ ,  $L = 1\mu\text{m}$ ,  $V_{DS} = 0.1\text{V}$ ,  $V_{tn} = 1\text{V}$ ,  $\mu_n C_{OX} = 25\mu\text{A/V}^2$ . 5M

(OR)

- Find the voltage gain of the common gate stage. 5M
- Obtain the ON resistance of an nMOS transistor with  $V_{GS} = 3\text{V}$ ,  $V_{tn} = 1\text{V}$ ,  $\mu_n C_{OX} = 25\mu\text{A/V}^2$ ,  $W = 3\mu\text{m}$  and  $L = 1\mu\text{m}$ . 5M

UNIT-IV

8 .a) Explain the design of a basic current mirror.

5M

b) What is the need if biasing? Analyse a CS biasing circuit.

5M

(OR)

9. Analyse a different pair with small signal inputs and find the differential gain.

10M

## Scheme of Examination

1.  $V_{BE} = 0.7V$
2. (a) Description of the three modes - 3m  
 Formulae for  $I_E$  to determine the Concentration - 2m  
 (b)  $V_{BE}, I_E \rightarrow 1m$   
 expression for  $I_E$  - 2m  
 value of  $I_E$  - 2m
3. (a) five equations -  $5 \times 1 = 5m$   
 (b) equations of  $r_i$  and  $r_o$  - 2m  
 finding the value  $\frac{r_i}{r_o}$  - 3m
4. (a) Description of the breakdown mechanism - 5m  
 (b)  $I$  &  $V$  relation in a diode - 1m  

$$\frac{I_2}{I_1} = e^{\frac{V_2 - V_1}{V_T}}$$
 - 2m  
 value of  $n$  - 2m
5. (a) Simple circuits of three configurations - 2m  
 Any three comparison - 3m  
 (b) circuit diagram - 1m  
 quiescent current value - 2m  
 $V_{CEQ}$  - 2m
6. (a) Schematic diagram - 2m  
 Description of the working principle - 3m  
 (b) for  $V_{GS} = 0V$  case  $\rightarrow 1m$   
 for  $V_{GS} = 1V$  case  $\rightarrow 1m$   
 for  $V_{GS} = 2V$  case  $\rightarrow 3m$
7. (a) circuit diagram - 2m  
 Small signal equivalent circuit along with the derivation of voltage gain - 3m  
 (b) quantification analysis of the large signal model to derive the voltage gain - 3m
8. (a) Diagram showing the design concept - 1m  
 circuit diagram - 2m  
 Description - 2m  
 (b) Need of biasing - 1m  
 circuit of CS biasing - 2m  
 Explanation - 2m
9. circuit of differential pair with small signal inputs - 2m  
 circuit for simplified analysis - 4m  
 Derivation of the gain - 4m

1. (a) Controlled addition of impurities to a crystal is called doping.  
 (b) The transport of charges in a crystal as a result of under the influence of an electric field is called drift current.

$$(c) P_{no} n_{no} = n_i n_v \exp\left(-\frac{E_g}{kT}\right) = n_i^2$$

$$(d) 4$$

(e) Common Collector Configuration

$$(f) \alpha = \frac{\beta}{1+\beta}$$

(g) It is the minimum gate voltage at which the conduction just starts & the inversion region is formed.

$$(h) \mu = q_m n_d$$

$$(i) -\frac{R_D}{R_S}$$

(j) It provides a large resistance without changing the biasing value.

2. (a) The basic kinds of energy band model are

- (i) Allowed energy states for electrons
- (ii) Distribution of allowed states over energy;  $N(E)$
- (iii) At any temperature  $T$ , under equilibrium only a fraction of allowed energy states are occupied. This fraction is given by  $f(E, T)$ , Fermi dirac function.

Allowed energy states for electrons

In the silicon crystal, as the atomic separation decreases, the 2N states of 3s orbital and 6N states of 3p orbital club together and split into two energy bands namely valence band (4N states) and conduction band (4N states).

The 4N electrons available occupy the valence band and the conduction band has empty states (at  $T=0K$ ).

 


Fig. Energy band model of semiconductor.

Distribution of allowed states over energy

$$N(E) = a_2 \sqrt{E - E_c}$$

where  $a_2 = \frac{2\sqrt{2} \pi m_p^{3/2}}{h^3}$

$$N(E) = a_1 \sqrt{E - E_v}$$

where  $a_1 = \frac{2\sqrt{2} \pi m_n^{3/2}}{h^3}$

Fermi Dirac fraction

$$f(E, T) = \frac{1}{1 + \exp\left(\frac{E - E_f}{kT}\right)}$$

under equilibrium where  $E_f$  = Fermi level

The information related to

- allowed energy states
- the density of states function
- the fraction of occupied states at an energy E

can be put together to derive an equation for the carrier concentration or intrinsic concentration.

$$n_i = \int_{E_c}^{E_T} N(E) dE f(E, T)$$

$$= \int_{E_c}^{E_T} a_1 \sqrt{E - E_c} \left[ \frac{1}{1 + \exp\left(\frac{E - E_f}{kT}\right)} \right] dE$$

The approximations used to easily evaluate the above integral are (i)  $E_T \rightarrow \infty$  (ii) Boltzmann approximation (iii) parabolic density of states approximation



After integration

$$n_i = 2 \left[ \frac{2\pi m_p kT}{h^2} \right]^{3/2} \exp \left( -\frac{E_i - E_f}{kT} \right)$$

$$= N_v \exp \left( -\frac{E_i - E_f}{kT} \right)$$

The number of holes in the valence band at any temperature is given by

$$p_i = \int_{E_B}^{E_V} N(E) dE \left[ 1 - f(E, T) \right]$$

$$= \int_{E_B}^{E_V} a_2 \sqrt{E_V - E} \left[ 1 - \frac{1}{1 + \exp \left( \frac{E - E_f}{kT} \right)} \right] dE$$

The approximations used to easily calculate the above integral are (i)  $E_B \rightarrow 0$  (ii) Boltzmann approximation (iii) parabolic density of states approximation

After integration

$$p_i = 2 \left[ \frac{2\pi m_p kT}{h^2} \right]^{3/2} \exp \left( -\frac{E_f - E_V}{kT} \right)$$

$$= N_v \exp \left( -\frac{E_f - E_V}{kT} \right)$$

2 (b) Given  $n_i = p_i$  and  $m_e = 2 m_p$

$$n_i = p_i$$

$$2 \left[ \frac{2 \pi m_e K T}{h^2} \right]^{3/2} \exp \left( -\frac{E_c - E_f}{K T} \right) = 2 \left[ \frac{2 \pi m_p K T}{h^2} \right]^{3/2} \exp \left( -\frac{E_f - E_v}{K T} \right)$$

As  $m_e = 2 m_p$  that gives

$$2^{3/2} \exp \left( -\frac{E_c - E_f}{K T} \right) = \exp \left( -\frac{E_f - E_v}{K T} \right)$$

$$\exp \frac{2 E_f - (E_c + E_v)}{K T} = 2^{-3/2}$$

$$\frac{2 E_f - (E_c + E_v)}{K T} = \ln 2^{-3/2}$$

$$E_f = \frac{E_c + E_v}{2} - \frac{3}{4} K T \ln 2$$

$$= \frac{E_c + E_v}{2} - 0.0135 \text{ eV}$$

Fermi level  $E_f$  is below the centre of bandgap by 0.0135 eV.

| 3 (a) Equation |           | Transport equation                                        |                                                                                                        |
|----------------|-----------|-----------------------------------------------------------|--------------------------------------------------------------------------------------------------------|
| Carrier flux   | Electrons | $J_n = q n \mu_n E + q D_n \frac{\partial n}{\partial x}$ | $\frac{\partial}{\partial t}(n) = \frac{1}{q} \frac{\partial J_n}{\partial x} + G - \frac{S n}{\tau}$  |
|                | Holes     | $J_p = q p \mu_p E - q D_p \frac{\partial p}{\partial x}$ | $\frac{\partial}{\partial t}(p) = -\frac{1}{q} \frac{\partial J_p}{\partial x} + G - \frac{S p}{\tau}$ |
| Electric flux  |           | $E = -\frac{\partial \psi}{\partial x}$                   | $\frac{\partial E}{\partial x} = \frac{\rho}{\epsilon}$                                                |

3(b)  $J$  is total current density

$$J_n = \frac{3}{4} J$$

$$J_p = \frac{1}{4} J$$

$$v_n = 3v_p$$

$$J_n = qn v_n$$

$$J_p = qp v_p$$

$$J = J_n + J_p$$

$$\frac{J_n}{J_p} = \frac{qn v_n}{qp v_p}$$

$$\frac{(3/4 J)}{(1/4 J)} = \frac{qn \cdot 3v_p}{qp v_p}$$

$$3 = \frac{n}{p} (3)$$

$$n = p$$

$$\frac{n}{p} = 1.$$



#### 4 (a) Avalanche breakdown

As the applied reverse bias increases, the field across the junction increases correspondingly.

Thermally generated carriers while traversing the junction acquire a large amount of kinetic energy from this field. As a result, the velocity of these carriers increase.

These electrons disrupt covalent bond by colliding with immobile ions and create new electron hole pairs.

These new carriers again acquire sufficient energy from the field and collide with other immobile ions thereby generating further electron hole pairs.

This process is cumulative in nature and results in generation of avalanche of charge carriers within a short time.

This mechanism of carrier generation is known as avalanche multiplication. This process results in flow of large amount of current at the same value of reverse bias.

4 (b) The current equation in a diode is

$$I = I_0 (e^{V/nV_T} - 1)$$

$$\approx I_0 e^{V/nV_T} \text{ for } V > 3V_T$$

$$\therefore I_1 = I_0 e^{V_1/nV_T}$$

$$I_2 = I_0 e^{V_2/nV_T}$$

$$\frac{I_2}{I_1} = e^{(V_2 - V_1)/nV_T}$$

$$\ln \left( \frac{I_2}{I_1} \right) = \frac{V_2 - V_1}{nV_T}$$

$$\ln \left( \frac{20 \times 10^{-3}}{0.6 \times 10^{-3}} \right) = \frac{(600 - 400) \times 10^{-3}}{n (0.026 \times 10^{-3})} \Rightarrow n = 1.097$$

# Comparison of Transistor Configurations



Fig: Common base Configuration



Fig: CE Configuration

 


Fig: CC Configuration

| Parameter                 | CB Configuration         | CE Configuration     | CC Configuration          |
|---------------------------|--------------------------|----------------------|---------------------------|
| Input dynamic resistance  | Very low ( $20\Omega$ )  | high ( $600\Omega$ ) | Very high ( $1M\Omega$ )  |
| Output dynamic resistance | Very high ( $1M\Omega$ ) | low ( $73.5\Omega$ ) | Very low ( $21.6\Omega$ ) |
| voltage gain              | 3330                     | -3330                | 1                         |
| Current gain              | less than unity (0.99)   | high (-50)           | high (51)                 |

when  $R_L = \infty$

3(b) Determine the quiescent currents and the collector to emitter voltage for a silicon transistor with  $\beta = 50$  in the self biasing arrangement. The circuit component values are  $V_{CC} = 20V$ ,  $R_C = 2k\Omega$ ,  $R_E = 0.1k\Omega$ ,  $R_1 = 100k\Omega$ ,  $R_2 = 5k\Omega$



$$V = \frac{R_E}{R_1 + R_2} V_{CC}$$

$$= \frac{5}{100 + 5} (20)$$

$$= 0.952 \text{ Volt}$$

$$R = R_1 || R_2$$

$$= \frac{(5k)(100k)}{5k + 100k}$$

$$= 4.76k$$



$$I_E = I_C + I_B$$

$$= \beta I_B + I_B$$

$$= (\beta + 1) I_B$$

$$0.952 = 4.76(10^3) I_B + (0.1 \times 10^3)(51) I_B$$

$$= (4760 + 5100) I_B$$

$$I_B = 96.6 \mu A$$

$$I_C = \beta I_B = 50(96.6) \times 10^{-6}$$

$$= 4.83 \text{ mA}$$

$$I_E = 4.896 \text{ mA}$$

$$20 = I_C R_C + V_{CE} + I_E R_E$$

$$20 = (4.8)(10^{-3})(2 \times 10^3) + V_{CE} + (4.896)10^{-3}(0.1 \times 10^3)$$

$$20 = 9.6 + V_{CE} + 0.489$$

$$V_{CE} = 20 - 10.089$$

$$= 9.91 \text{ V}$$

6/2/

## Enhancement MOSFET (Metal Oxide Semiconductor Field Effect Transistor):

The n-channel MOSFET consists of a lightly doped p-type substrate into which two highly doped n<sup>+</sup> regions are diffused, as shown in the following fig

 


Fig. Enhancement n-channel MOSFET

The insulating layer of silicon dioxide is the reason why this device is called the insulated gate field effect transistor.

If a positive voltage is applied to the gate w.r.t the body or substrate, at the surface the material becomes less p-type for small +ve voltage.

If the gate voltage (+ve) is increased further, the surface first becomes space charge neutral and next it becomes negatively charged excessively, which means that the surface becomes n-type for large values of gate voltage. This is called inversion of p-type material becomes n-type at the surface with the applied +ve gate voltage.

This is shown in the following diagram.

 


Fig: Schematic of MOSFET when gate is applied a +ve voltage w.r.t substrate.


The depth of the conductive channel can be varied by varying the gate voltage.

The gate voltage that is necessary to make the surface of the semiconductor as conductive as the substrate or bulk or body is called threshold voltage ( $V_T$ ).

(or)

Threshold voltage is that gate voltage that will permit a certain amount of current to flow from source to drain.

 As the drain current is enhanced by the +ve gate voltage, this device is called an enhancement type MOSFET.



$$V_{GD} = V_{GS} - V_{DS}$$

Fig: MOSFET Schematic when  $V_{DS} = V_{GS} - V_T$

When only the threshold voltage is applied, the channel gets formulated. The channel depth is dependent upon the excess voltage over and above  $V_T$ .

Initially the depth of the channel is dependent on  $V_{GS} - V_T$ . If  $V_{DS}$  is increased from zero, the depth of the channel at the drain end decreases. This is shown in the above fig.

If  $V_{DS}$  is increased to a value  $V_{GS} - V_T$  then the channel gets closed at the drain end & the channel is pinched off at the drain end.

The characteristics of MOSFET are shown below.

 


Fig: Drain characteristics of MOSFET

 


Fig: Transfer characteristics.

In the Saturation region,  $I_D = K (V_{GS} - V_T)^2$  where  $K = \text{Constant}$

In the Triode region,  $I_D = 2K \left[ (V_{GS} - V_T) V_{DS} - \frac{V_{DS}^2}{2} \right]$

G (b)

For  $V_{GS} = 0V < V_{th} = 1V$ , channel does not form,  $I_D = 0$

For  $V_{GS} = 1V = V_{th}$ , channel does not form,  $I_D = 0$

For  $V_{GS} = 2V > V_{th} = 1V$ , channel forms and the equation of

$I_D$  is

$$I_D = \mu_n C_{ox} \frac{W}{L} \left[ (V_{GS} - V_{th}) V_{DS} - \frac{V_{DS}^2}{2} \right]$$

$$= 25 \times 10^{-6} \frac{5}{1} \left[ (2-1) 0.1 - \frac{(0.1)^2}{2} \right]$$

$$= 11.875 \mu A$$



## Voltage gain of a common gate stage



Fig: (a) Common gate stage with direct coupling at input  
(b) CG stage with capacitive coupling at input.

A common gate stage senses the input at the source and produces the output at the drain.

The gate is connected to a dc voltage to establish proper operating conditions.

First consider the large signal behavior of the circuit shown in fig a.

For simplicity, assume that  $v_{in}$  decreases from a large positive value. Also  $\lambda = 0$ .

For  $V_{in} \geq V_b - V_{TH}$ ,  $M_1$  is OFF and  $V_{out} = V_{DD}$

For lower values of  $V_{in}$ ,

$$I_D = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_b - V_{in} - V_{TH})^2 \quad \text{if } M_1 \text{ is in saturation}$$

As  $V_{in}$  decreases, so does  $V_{out}$ , eventually driving  $M_1$  into the triode region

$$V_{DD} - \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_b - V_{in} - V_{TH})^2 R_D = V_b - V_{TH}$$

The input-output relation is shown in the above fig, illustrating the case in which  $M_1$  enters the triode region as  $V_{in}$  decreases.

In the region where  $M_1$  is saturated,

$$V_{out} = V_{DD} - \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_b - V_{in} - V_{TH})^2 R_D$$

obtaining a small signal gain of

$$\frac{\partial V_{out}}{\partial V_{in}} = -\mu_n C_{ox} \frac{W}{L} (V_b - V_{in} - V_{TH}) \left( -1 - \frac{\partial V_{TH}}{\partial V_{in}} \right) R_D$$

$$\text{Since } \frac{\partial V_{TH}}{\partial V_{in}} = \frac{\partial V_{TH}}{\partial V_{SB}} = \eta, \text{ we have } \frac{\partial V_{out}}{\partial V_{in}} = \mu_n C_{ox} \frac{W}{L} R_D (V_b - V_{in} - V_{TH}) (1 + \eta)$$

$$= g_m (1 + \eta) R_D$$

Interestingly, the body effect increases the equivalent transconductance of the stage.

 


Fig: Common gate input-output characteristics

7(b)

Given nMOS Transistor

$$V_{GS} = 3V$$

$$V_{TH} = 1V$$

$$\mu_n C_{ox} = 25 \mu A/V^2$$

$$W = 3 \mu m$$

$$L = 1 \mu m$$

$$\frac{\partial I_D}{\partial V_{DS}} = \mu_n C_{ox} \frac{W}{L} \left[ (V_{GS} - V_{TH}) - V_{DS} \right]$$

$$\left. \frac{\partial I_D}{\partial V_{DS}} \right|_{V_{DS} \rightarrow 0} = \mu_n C_{ox} \frac{W}{L} (V_{GS} - V_{TH})$$

$$g_{m,ON} = \frac{\partial I_D}{\partial V_{DS}} = \frac{1}{\mu_n C_{ox} \left( \frac{W}{L} \right) (V_{GS} - V_{TH})}$$

$$= \frac{1}{25 \times 10^{-6} \left( \frac{3}{1} \right) (3-1)} \cdot \frac{A}{V} \cdot \frac{\mu m}{\mu m} V$$

$$= 6.67 k\Omega$$

2(a)

Design of a basic current mirror.

The design of current sources in analog circuits is based on "copying" currents from a reference, with the assumption that one precisely defined current source is already available.



Fig: Use of a reference to generate various currents

Two identical MOS devices that have equal gate source voltages and operate in saturation carry equal currents (if  $\lambda = 0$ )

 


Fig: Basic current mirror

The structure consisting of  $M_1$  and  $M_2$  in the above fig is called a "current mirror". In the general case, the transistors need not be identical. Neglecting the channel length modulation, we can write

$$I_{REF} = \frac{1}{2} \mu_n C_{ox} \left( \frac{W}{L} \right)_1 (V_{GS} - V_{TH})^2$$

$$I_{out} = \frac{1}{2} \mu_n C_{ox} \left( \frac{W}{L} \right)_2 (V_{GS} - V_{TH})^2$$

obtaining 
$$I_{out} = \frac{(W/L)_2}{(W/L)_1} I_{REF}$$

Ref:

Kind of biasing

The amplifier stages must be properly biased so that, in the absence of the input signal, each transistor carries the required current and sustains the necessary terminal voltages.

The current establishes the transconductance and output resistance of the transistor while the terminal voltages determine the headroom and hence the allowable voltage swings.

CS biasing: Simple CS stage



Fig: CS biasing: Simple CS stage

$V_{in}$  is coupled capacitively to establish a high impedance to  $V_B$  so that  $x$  has the same voltage/dc voltage as  $V_B$  and the same signal voltage as  $V_{in}$ .

Note that  $C_B$  and  $R_B$  form a high pass filter, select  $\frac{1}{2\pi R_B C_B}$  lower than the lowest input frequency so that the ac gain from  $V_{in}$  to  $V_x$  is near unity in the frequency range of interest.

9.

Analysis of a differential pair with small signal inputs to find the differential gain.

 


Fig 1 Differential pair with small signal inputs.

Assume that  $M_1$  and  $M_2$  are saturated

Assume that  $R_{D1} = R_{D2} = R_D$

The above circuit is driven by two independent signals - thus, the output can be computed by superposition.

 


Fig 2(a) Differential pair sensing one input signal  
 (b) circuit of (a) viewed as a CS stage degenerated by  $M_2$   
 (c) equivalent of circuit (b).

Let us set  $v_{in2}$  to zero and find the effect of  $v_{in1}$  at  $x$  and  $y$  [fig 2(a)].

To obtain  $v_x$ , note that  $M_1$  forms a common source stage with a degeneration resistance equal to the impedance seen looking into the source of  $M_2$  [fig 2(b)].

Neglecting the channel length modulation and body effect,  
 $R_S = \frac{1}{g_{m2}}$  [fig 2(c)] and

$$\frac{V_x}{V_{in1}} = \frac{-R_D}{\frac{1}{g_{m1}} + \frac{1}{g_{m2}}}$$

To calculate  $V_y$ , note that  $M_1$  drives  $M_2$  as a source follower and replace  $V_{in1}$  and  $M_1$  by a Thevenin equivalent (b93)



Fig 3: Replacing  $M_1$  by a Thevenin equivalent

The Thevenin voltage  $V_T = V_{in1}$  and

the resistance  $R_T = \frac{1}{g_{m1}}$

Hence  $M_2$  operates as a common gate stage, exhibiting a gain of

$$\frac{V_y}{V_{in1}} = \frac{R_D}{\frac{1}{g_{m2}} + \frac{1}{g_{m1}}}$$

It follows from the earlier two equations that the overall voltage gain for  $V_{in1}$  is

$$(V_x - V_y) \Big|_{\text{due to } V_{in1}} = \frac{-2R_D}{\frac{1}{g_{m1}} + \frac{1}{g_{m2}}} V_{in1}$$

$$= -g_m R_D V_{in1} \quad \text{where } g_{m1} = g_{m2} = g_m$$

By virtue of symmetry, the effect of  $V_{in2}$  at  $x$  and  $y$  is identical to that of  $V_{in1}$  except for a change in the polarities.

$$(V_x - V_y) \Big|_{\text{due to } V_{in2}} = g_m R_D V_{in2}$$

By superposition 
$$\frac{(V_x - V_y)_{\text{tot}}}{V_{in1} - V_{in2}} = -g_m R_D$$