

Bapatla Engg College : Bapatla.

Dept of EIE, 2/4 EIE RE

Sub code 18EI304

Sub: Network Theory

2/4 EIE, 3rd Sem

Max Marks: 50.

1. Answer all questions

- a) Energy is the capacity for doing work. Energy is nothing but stored work.

Energy is measured in Joules (J)

Power is the rate of change of energy

$$\text{Power} = \frac{\text{Energy}}{\text{Time}} = \frac{W}{t}$$

Power is measured in Watts (W)

- b) Independent sources for which voltage and current are independent and are not affected by other parts of the circuit. In case of dependent source the source voltage or current is not fixed, but is dependent on the voltage and current existing at some other location in the circuit.

c)
$$\text{Crest factor} = \frac{\text{Peak value of wave}}{\text{RMS value of wave}} = \frac{V_p}{V_{rms}}$$

$$\text{Form factor} = \frac{\text{RMS value of wave}}{\text{Avg value of wave}} = \frac{V_{rms}}{V_{av}}$$

d) The phase of a sine wave is an angular measurement that specifies the position of the sine wave relative to a reference.
If we draw wave forms for both voltage and current at different positions we can observe the phase difference b/w two wave forms.

e) In any linear N/W, if a single voltage V_a in branch 'a' produces a current I_b in branch 'b'. Then if the vol source V_a is removed and inserted in branch 'b' will produce a current I_b in branch 'a'. The ratio of response to excitation is same for the two conditions mentioned above. This is called the reciprocity theorem.

f) In a series RLC Ckt, series resonance occurs when $X_L = X_C$. The freq at which the resonance occurs is called resonant freq.

$$f_r = \frac{1}{2\pi\sqrt{LC}}$$

g) The response changes with time, gets saturated after some time and is referred to as the transient response.
A ckt having const sources is said to be in steady state if the currents and voltages do not change with time.

h) LT of Unit ramp function is $\frac{1}{s^2}$




i) 1. Diff 2. Integration 3. Translation 4. scale change etc.

j) $Z_{11} = \frac{V_1}{I_1} \Big|_{I_2=0}$ $Z_{12} = \frac{V_1}{I_2} \Big|_{I_1=0}$ $Z_{21} = \frac{V_2}{I_1} \Big|_{I_2=0}$ $Z_{22} = \frac{V_2}{I_2} \Big|_{I_1=0}$

Unit - I

2 a)


(5M)

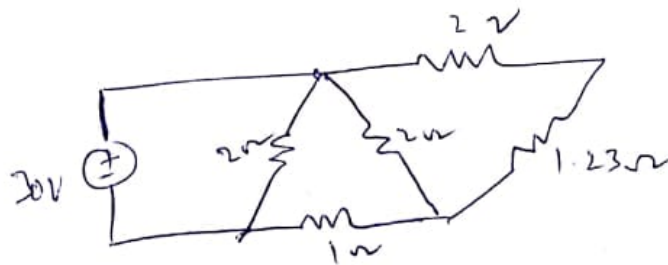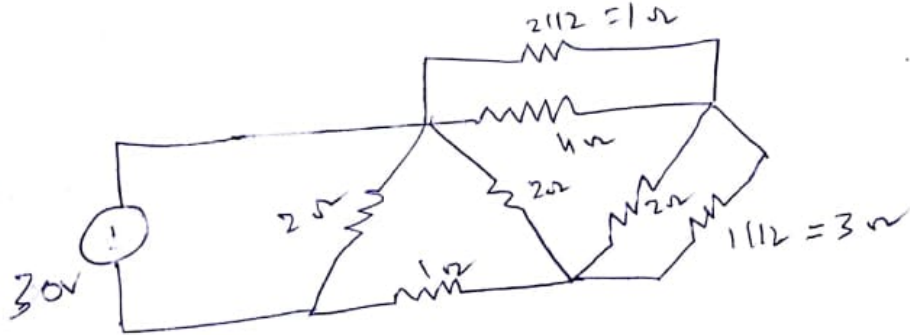
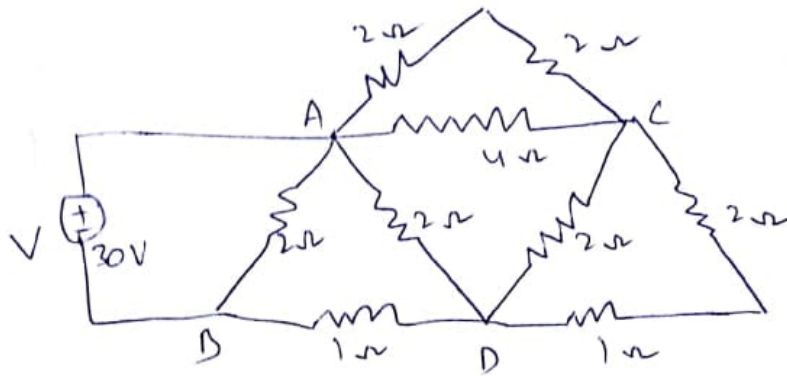


current delivered by the source

$$= \frac{30}{1.05} = 28.57 \text{ A}$$

b)

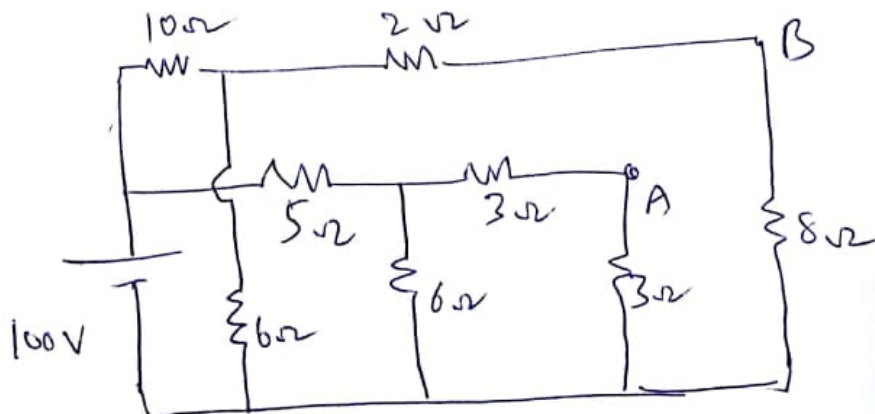

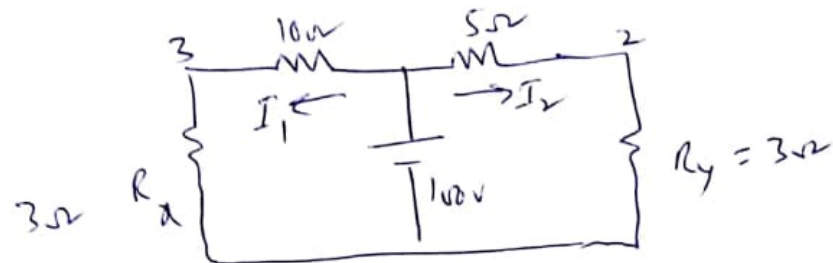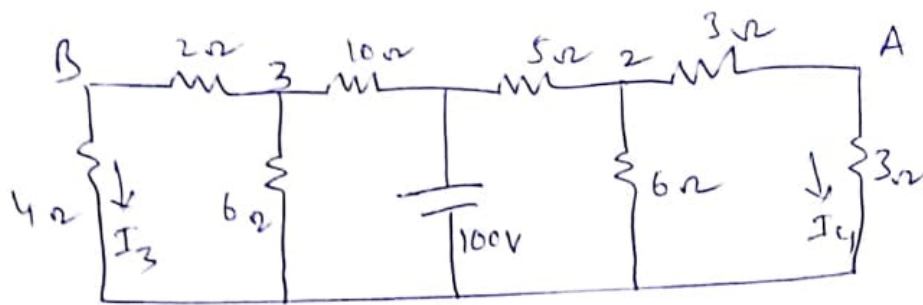

$$R_x = (2 + 4) \parallel 6 = 3\Omega \quad R_y = (3 + 3) \parallel 6 = 3\Omega$$

$$I_1 = \frac{100}{13} = 7.69A \quad I_2 = \frac{100}{8} = 12.5A$$

$$I_3 = 7.69 \times \frac{6}{12} = 3.845A$$

$$I_4 = 12.5 \times \frac{6}{12} = 6.25A$$

$$V_{AB} = V_A - V_B$$


$$V_A = I_4 \times 3 = 6.25 \times 3 = 18.75V$$

$$V_B = I_3 \times 4 = 3.845 \times 4 = 15.38V$$

$$V_{AB} = 18.75 - 15.38 = 3.37V$$

SM

3. a)

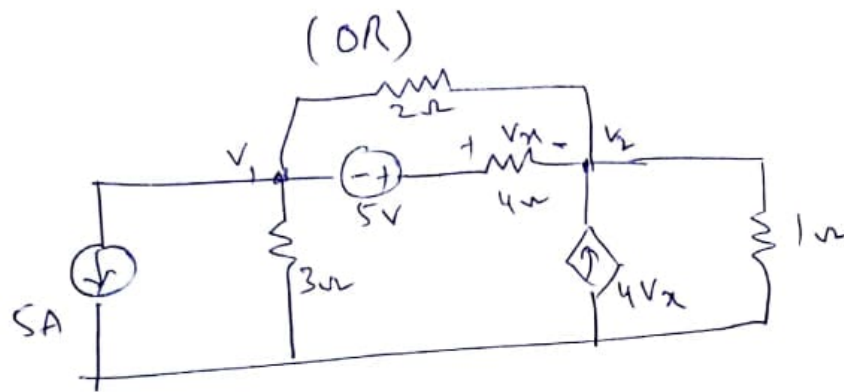

By applying KCL at node V_1

$$5 + \frac{V_1}{3} + \frac{V_1 - V_2}{2} + \frac{V_1 + 5 - V_2}{4} = 0 \quad \text{--- (1)} \quad 1M$$

At node V_2

$$\frac{V_2 - 5 - V_1}{4} + \frac{V_2 - V_1}{2} - 4V_x + \frac{V_2}{1} = 0 \quad \text{--- (2)} \quad 1M$$


$$V_x = V_1 + 5 - V_2 \quad \text{--- (3)} \quad 1M$$

By solving (1), (2) and (3)

$$V_1 = -7.535V \quad V_2 = -2.54 \quad 2M$$

$$V_x = -0.01V.$$

b)

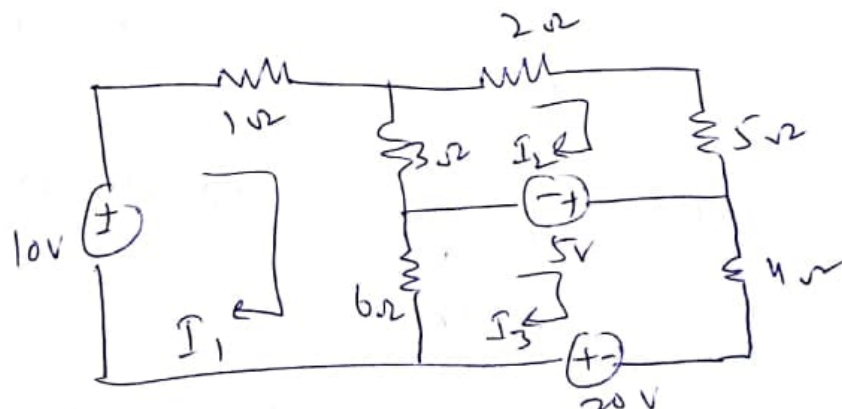

$$-10 + I_1 + 3(I_1 - I_2) + 6(I_1 - I_3) = 0$$

$$10I_1 - 3I_2 - 6I_3 = 10V \quad \text{--- (1)} \quad 1M$$

$$2I_2 + 5I_2 + 5 + 3(I_2 - I_1) = 0$$

$$-3I_1 + 10I_2 = -5 \text{ V} \quad \text{--- (2)}$$

$$-5 + 4I_3 - 20 + 6(I_3 - I_1) = 0$$

$$-6I_1 + 10I_3 = 25 \text{ V} \quad \text{--- (3)}$$

$$I_1 = 4.27 \text{ A} \quad I_2 = 0.78 \text{ A} \quad I_3 = 5.06 \text{ A}$$


$$\text{Voltage across } 6\Omega \text{ is } = I_2 \times 6 = -3 \text{ V}$$

$$\underline{\text{Unit} - \Pi}$$

4a)

$$\text{Form factor} = \frac{V_{rms}}{V_{av}}$$
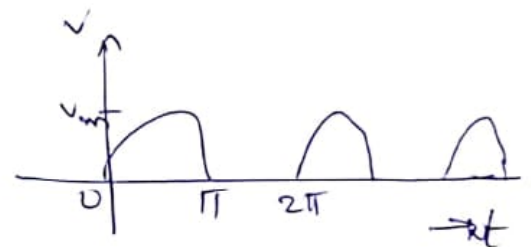
$$\text{crest factor} = \frac{V_m}{V_{rms}}$$



$$V = V_m \sin \omega t \quad 0 < \omega t < \pi$$

$$= 0 \quad \pi < \omega t < 2\pi$$

$$V_{av} = \frac{1}{2\pi} \int_0^\pi V_m \sin \omega t \, d(\omega t)$$

$$= 0.318 V_m$$

$$V_{rms} = \frac{V_m}{2}$$

$$\text{Form factor} = \frac{V_m/2}{0.318 V_m} = 1.572$$

$$\text{crest factor} = \frac{V_m}{0.318 V_m/2} = \frac{2}{0.318} = 6.31$$


2M

4.6)

$$\text{Average Power} = \frac{1}{t_2 - t_1} \int_{t_1}^{t_2} P(t) dt$$

$$P_{av} = V_{eff} I_{eff} \cos \theta$$
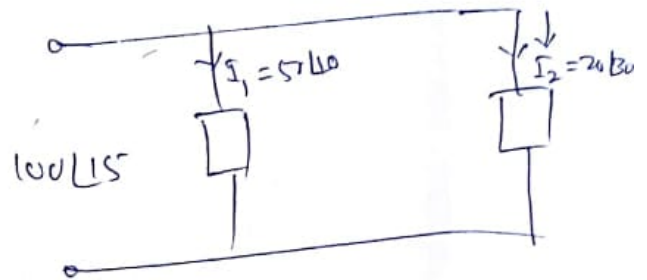
$$\text{Reactive power } P_r = V_{eff} I_{eff} \sin \theta \text{ VAR}$$



$$Z_1 = \frac{100 \angle 15^\circ}{50 \angle 10^\circ} = 1.99 + j0.174 \Omega$$

$$Z_2 = \frac{100 \angle 15^\circ}{20 \angle 30^\circ} = 5 \angle -15^\circ = 4.83 - j1.29 \Omega$$

$$\text{True power in } Z_1 \text{ is } P_{t1} = I_1^2 R = (50)^2 \times 1.99 = 4975 \text{ W}$$

$$\text{Reactive power in } Z_1 \text{ is } P_{r1} = I_1^2 X_L = (50)^2 \times 0.174 = 435 \text{ VAR}$$

$$\text{Apparent power in } Z_1 \text{ is } P_{a1} = I_1^2 Z_1 = (50)^2 \times 2 = 5000 \text{ VA}$$

$$\text{True power in } Z_2 \text{ is } P_{t2} = I_2^2 R = (20)^2 \times 4.83 = 1932 \text{ W}$$

$$\text{Reactive power in } Z_2 \text{ is } P_{r2} = I_2^2 X_c = -(20)^2 \times 1.29 = -516 \text{ VAR}$$



$$\text{Apparent power in } Z_2 \text{ is } P_a = I_2^2 Z_2 = (20)^2 \times 5 = 2000 \text{ VA}$$

(OR)

5 a) Super position Theorem
statement — 2 M

Super position Theorem
proof with example — 3 M

b)

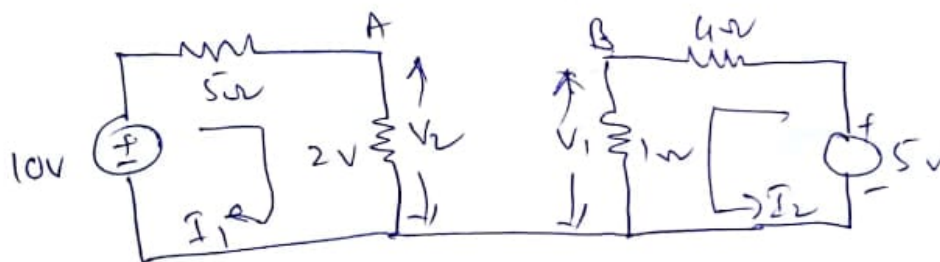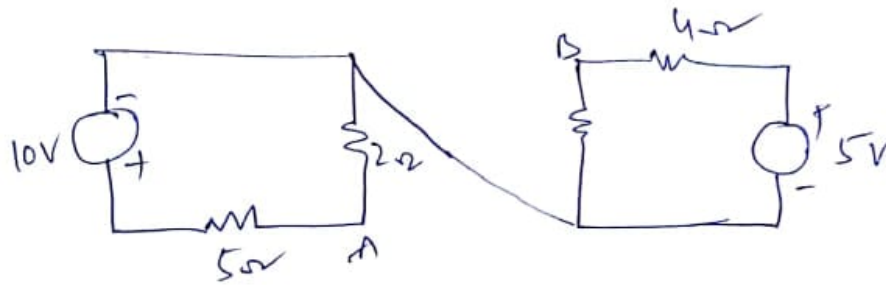

$$V_{AB} = V_2 + V_1$$

$$V_{AB} = V_2 - V_1$$
$$= 2.85 - 1 = 1.85V$$


$$V_2 = 2 \times \frac{10}{7} = 2.85$$

$$V_1 = 1 \times \frac{5}{5} = 1V$$

Theremin's Resistance b/w AB

$$R_{AB} = (5 \parallel 2) + (4 \parallel 1) = 1.43 + 0.8 = 2.23\Omega$$

Theremin's equivalent circuit

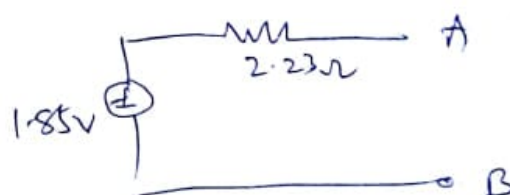

6 a) RLC series resonance ckt



Derivations

$$f_0 = \frac{1}{2\pi\sqrt{LC}}$$

$$BW = \frac{R}{2\pi L}$$

$$Q = \frac{f_2}{f_2 - f_1}$$

$$f_1 = f_0 - \frac{R}{4\pi L}$$

$$f_2 = f_0 + \frac{R}{4\pi L}$$

6 b)

$$L = 0.1 \text{ H}$$

$$Q = 5$$


$$\omega_0 = 50 \text{ rad/sec}$$

$$Q = \frac{\omega_0 L}{R} = \frac{50 \times 0.1}{R}$$

$$R = \frac{50 \times 0.1}{5} = 1 \Omega$$

$$\omega_0^2 = \frac{1}{LC} \quad (50)^2 = \frac{1}{(0.1) \times C}$$
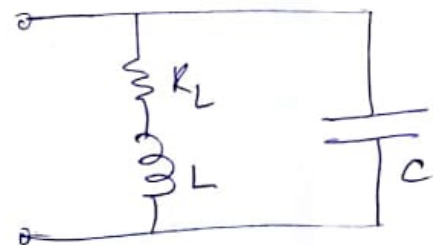
$$C = \frac{1}{(0.1) \times (50)^2} = 40 \text{ mF}$$



7 a) DC response of RL & RC ckt

RL ckt



$$V = Ri + L \frac{di}{dt}$$

$$\frac{di}{dt} + \frac{R}{L}i = \frac{V}{L}$$

$$i = C e^{-\frac{R}{L}t} + \frac{V}{R}$$

$$t=0 \quad \dot{i}=0 \quad C = \frac{V}{R}$$
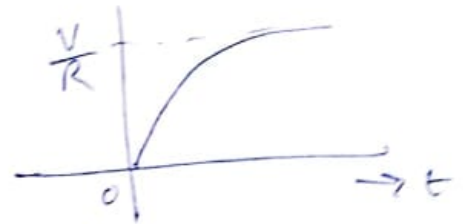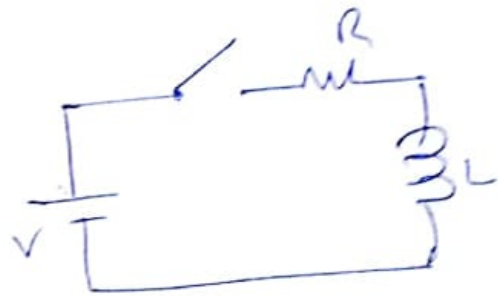
$$i = \frac{V}{R} (1 - e^{-\frac{R}{L}t})$$



RC circuit



$$V = Ri + \frac{1}{C} \int i dt$$

$$\frac{di}{dt} + \frac{i}{RC} = 0$$


$$i = C e^{-t/RC}$$

$$t=0 \quad i = \frac{V}{R} \quad C = \frac{V}{R}$$

$$i = \frac{V}{R} e^{-t/RC}$$

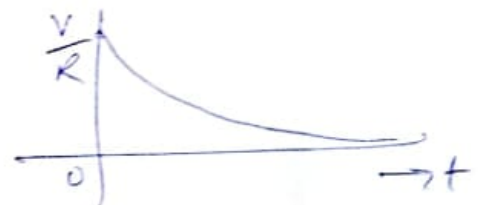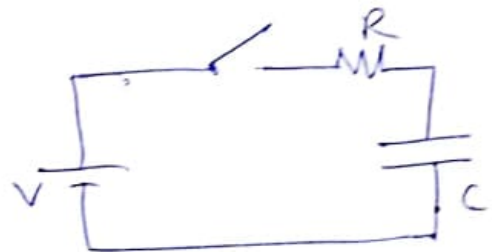

7 b)

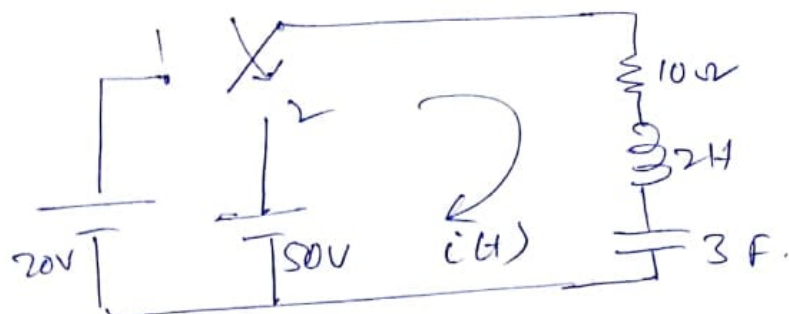

$$50 = 10i + 2 \frac{di}{dt} + \frac{1}{3} \int i dt$$

$$\frac{d^2 i}{dt^2} + 5 \frac{di}{dt} + \frac{i}{6} = 0.$$

$$D_1, D_2 = \frac{-5}{2} \pm \sqrt{\left(\frac{5}{2}\right)^2 - \frac{1}{6}}$$

$$= -2.5 \pm 2.47 = -0.03, -4.97$$

Solution $i = C_1 e^{-0.03t} + C_2 e^{-4.97t}$

$t=0 \quad i=0 \quad C_1 + C_2 = 0$

$t=0 \quad L \frac{di}{dt} = 50 \quad \frac{di}{dt} = 25.$

$$\frac{di}{dt} = -0.03 C_1 e^{-0.03t} - 4.97 C_2 e^{-4.97t}$$

$$25 = -0.03 C_1 - 4.97 C_2$$

$$C_1 = 5.06 \quad C_2 = -5.06$$

$$i(t) = 5.06 e^{-0.03t} - 5.06 e^{-4.97t}$$

Unit IV

8. a) Initial value theorem
statement

$$\lim_{t \rightarrow 0} f(t) = \lim_{s \rightarrow \infty} s F(s) \quad -1m$$

Initial value theorem

Proof

— $1\frac{1}{2}M$

Final value theorem

statement

— $1M$

$$\lim_{t \rightarrow \infty} f(t) = \lim_{s \rightarrow 0} s F(s)$$

Final value theorem

Proof.

— $1\frac{1}{2}M$

8 b)

Laplace Transform

i) $f(t) = (t+2)^2 e^t$

$$\begin{aligned} L[f(t)] &= L[(t^2 + 4 + 2t)e^t] \\ &= L[t^2 e^t + 4e^t + 2t e^t] \end{aligned}$$

$$= \frac{2}{(s-1)^3} + \frac{4}{s-1} + \frac{2}{(s-1)} \checkmark$$

ii) $f(t) = (2 - 2e^{-2t})$

let $f_1(t) = 2 - 2e^{-2t}$

$$L[f_1(t)] = \frac{2}{s} - \frac{2}{s+2} = \frac{4}{s(s+2)}$$

$$L\left[\frac{2-2e^{-2t}}{t}\right] = \int_0^\infty F_1(s) ds = \int_0^\infty \frac{4}{s(s+2)} ds$$

$$\frac{4}{s(s+2)} = \frac{A}{s} + \frac{B}{s+2} = \frac{2}{s} - \frac{2}{s+2}$$

$$\mathcal{L}\left\{\frac{2 - 2e^{-2t}}{t}\right\} = \int_0^{\infty} \mathcal{L}\left[2 - 2e^{-2t}\right] ds.$$

$$= \int_0^{\infty} \frac{2}{s} ds - \int_0^{\infty} \frac{2}{s+2} ds.$$

$$= -2 \log \left[\frac{s}{s+2} \right]$$

$$\mathcal{L}\left\{\frac{2 - 2e^{-2t}}{t}\right\} = 2 \log \left(\frac{s+2}{s} \right).$$

9. a)

$$10 = 4i + 2 \frac{di}{dt}$$

$$2 \frac{di}{dt} + 4i = 10$$

$$\cancel{2sI + 4} = \frac{10}{s} \quad 2[sI + 2] + 4I = \frac{10}{s}$$

$$\frac{10}{s} - 4I - 2sI + 2 = 0$$

$$10 - 4sI - 2s^2I + 2s = 0$$

$$I = \frac{10 + 2s}{2s(s+2)}$$


$$I = \frac{k_1}{s} + \frac{k_2}{s+2}$$


$$k_1 = \frac{5}{2}$$

$$k_2 = -\frac{3}{2}$$

$$I = \frac{5/2}{s} + \frac{-3/2}{s+2}$$
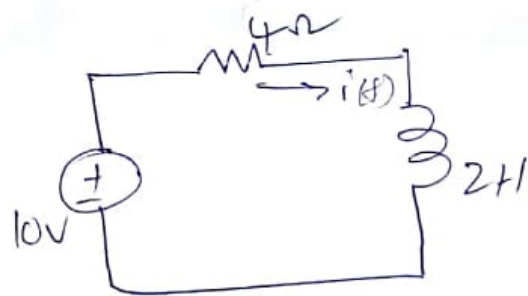
$$i(t) = \frac{5}{2} - \frac{3}{2} e^{-2t}.$$



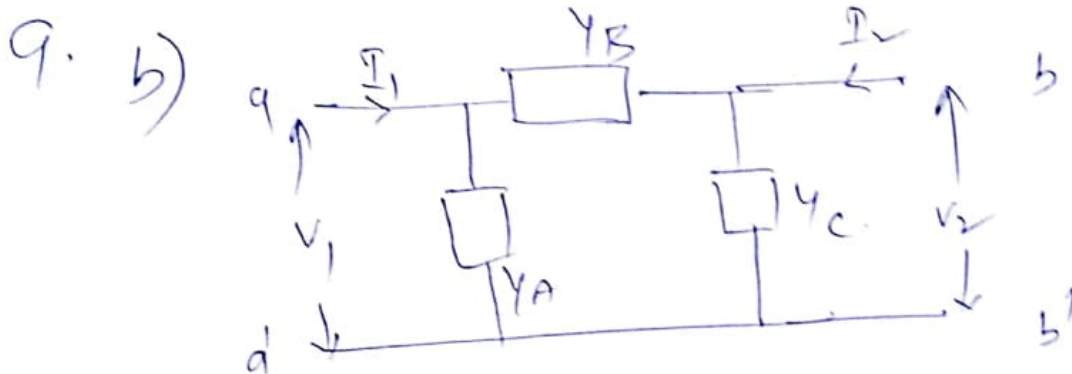

Y Parameters

$$Y_{11} = \frac{I_1}{V_1} \Big|_{V_2=0} = Y_A + Y_B$$

$$Y_{21} = \frac{I_2}{V_1} \Big|_{V_2=0} = -Y_B$$

$$Y_{22} = \frac{I_2}{V_2} \Big|_{V_1=0} = Y_B + Y_C$$

$$Y_{12} = \frac{I_1}{V_2} \Big|_{V_1=0} = -Y_B$$

$$I_1 = (Y_A + Y_B) V_1 - Y_B V_2$$

$$I_2 = -Y_B V_1 + (Y_C + Y_B) V_2$$

—2½m

→ Parameters

$$Z_{11} = \frac{Y_{22}}{\Delta Y}$$

$$Z_{12} = \frac{-Y_{12}}{\Delta Y}$$

$$Z_{21} = \frac{-Y_{21}}{\Delta Y}$$

$$Z_{22} = \frac{Y_{11}}{\Delta Y}$$

$$Y_{11} = Y_A + Y_B$$

$$Y_{12} = -Y_B$$

$$Y_{21} = -Y_B$$

$$Y_{22} = Y_B + Y_C$$

$$\Delta Y = Y_{11}Y_{22} - Y_{21}Y_{12}$$

$$-2\frac{1}{2}M$$