



Bapatla Engineering College :: Bapatla
(Autonomous)

Department of Information Technology

II -Mid Term Examination

Date: 5-02-2021	Sub. Code: 18IT204 (Semester-II)	Max.: 25 Marks
Class: I/IV B.Tech, SEC: IT-A&B	Sub: DLD	Time: 90 Min

Answer Question No.1 compulsorily.

(5*1=5 marks)

*Answer **ONE** question from each unit.*

(2*10=20 marks)

1. Answer all questions.

- a) how does ripple counter differ from synchronous counter
- b) compare combinational and sequential circuits
- c) how many flip flops are require to build MOD-12 counter
- d) Difference between flip flop and register .
- e) What is PLA?
- f) What are different types of RAM?

UNIT-III

2 a) Derive D flip flop and JK flip flop from T flip flop . Give the procedure for flip flop conversion

5M

b Explain about JK Flip flop with neat diagram and characteristic table and Excitation table

5M

(or)

3 Explain about SR flip flop with its truth table. Write its characteristic table, excitation table and characteristic equation . Draw its logic diagram

10M

(Or)

4 a) Explain about 3-bit binary down ripple counter

5M

b) Explain the working of bi-directional shift register with a neat diagram

5M

(or)

5 a) Explain about RAM and ROM , PROM, EEROM

5M

b) implement the following Boolean function using PAL

$$F(A,B,C,D)=m(4,5,6,10,11,12,14)$$

5M