

--	--	--	--	--	--	--	--

I/IV B.Tech (Regular/Supplementary) DEGREE EXAMINATION

August, 2023

Electrical and Electronics Engineering

Second Semester

CIRCUIT THEORY

Time: Three Hours

Maximum: 70 Marks

Answer question 1 compulsory.

(14X1 = 14Marks)

Answer one question from each unit.

(4X14=56 Marks)


- 1 a) State Ohm's law.
- b) Define passive circuit, give an example.
- c) Define form factor
- d) What are advantages of sinusoidal waveform in electrical systems?
- e) Define mesh
- f) Define Supernode
- g) What is meant by phase difference?
- h) Draw the phasor diagram for series RL circuit
- i) State compensation theorem.
- j) Write the condition for maximum power in maximum power transfer theorem.
- k) State Tellegen's theorem.
- l) What is the value of impedance at resonance?
- m) What is Band width in series resonance?
- n) Define Q-factor of an electrical network.

CO	BL	M
CO1	L2	1
CO1	L1	1
CO1	L1	1
CO2	L1	1
CO2	L1	1
CO2	L1	1
CO3	L1	1
CO3	L2	1
CO4	L2	1
CO4	L2	1
CO1	L2	1
CO1	L1	1
CO1	L1	1
CO2	L1	1

Unit-I

- 2 a) State and Explain KVL & KCL with an example.
- b) Find the source current in the resistance network shown below by using star-delta transformation.


CO1	L2	7M
CO1	L1	7M

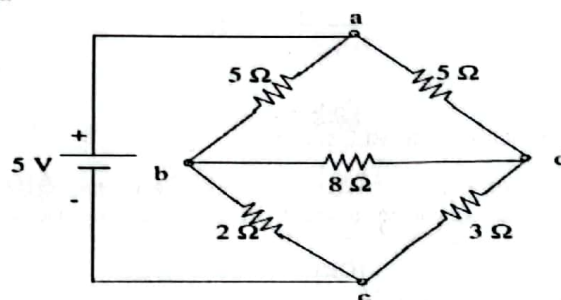

(OR)

- 3 a) Find average & RMS values of the waveform shown below.

CO1	L1	7M
-----	----	----

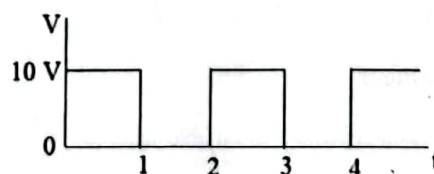


- b) An impedance $Z_1 = (6+j8) \Omega$ is connected in series with a parallel combination of impedances $Z_2 = (10+j6) \Omega$, $Z_3 = (8-j10) \Omega$ and is connected to a 300V, 50Hz supply. Find the total active power, reactive power & power factor of the circuit.

CO1	L2	7M
-----	----	----

Unit-II


- 4 a) What is the magnitude of current drained from the 10V source in the given circuit?

CO2	L1	7M
-----	----	----

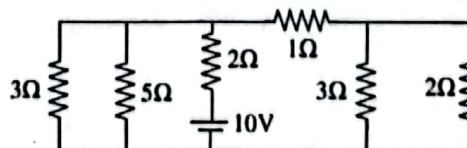


- b) Determine V in the circuit shown in figure.

CO2	L3	7M
-----	----	----

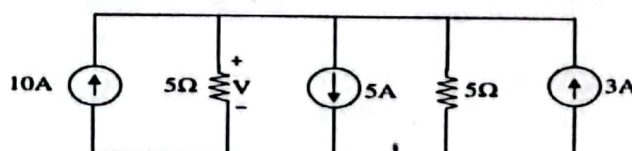

P.T.O.

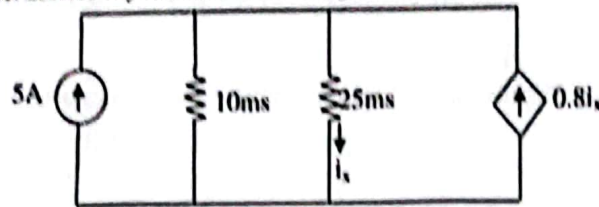- (OR)
- 5 a) Explain RL series circuit with pulse excitation. CO2 L2 7M
 b) Find the power absorbed by each element for the given circuit. CO2 L1 7M




Unit-III


- 6 a) State Thevenin's theorem. Write any two advantages of this theorem. CO3 L1 4M
 b) State and prove Maximum power transfer theorem for AC and DC excitations CO3 L2 10M

(OR)

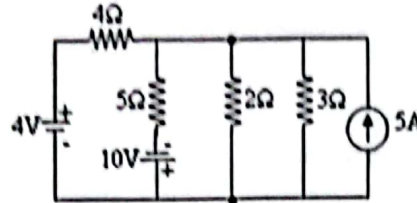- 7 a) Find the current through 2Ω resistor for given circuit using Norton's theorem. CO3 L1 7M



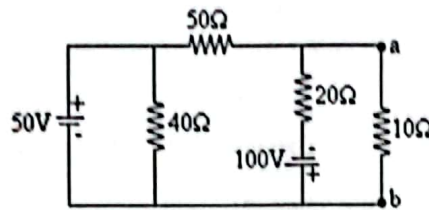- b) Find voltage across 10Ω resistance in the network shown below by using Superposition theorem. CO3 L2 7M




Unit-IV

- 8 a) Derive an expression for Bandwidth of Series RLC circuit. CO4 L3 7M
 b) An RLC Series circuit consists of $R=1k\Omega$, $L=100mH$, $C=10\mu F$. If a voltage of 100V is applied across the combination, determine resonant frequency, quality factor and bandwidth. CO4 L2 7M

(OR)

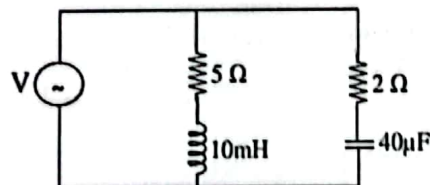- 9 a) Find the resonant frequency for the given circuit. CO4 L1 7M



- b) Deduce the current locus diagram of RL series circuit with L as variable parameter. CO4 L3 7M



Scheme of Evaluation:-

I/IV B-Tech Reg Exam.

Sub code:- 20EE205 Sub:- CIRCUIT THEORY 'Max Marks:- 70M.
ONE MARK QUESTIONS: 14 x 1 = 14M.

1(a) ohms Law:-

Ohms Law states that the voltage across a conductor is directly proportional to current flowing through it provided. all physical cond + temperature remain constant.

$$V = IR.$$

(b) Passive circuit is that donot require any external power source to operate. They can store or dissipate energy.

Ex:- Resistor, Inductor, Capacitor.

(c) Form factor = $\frac{\text{RMS value.}}{\text{Average value.}}$

(d) Advantages of sinusoidal waveform in electrical systems:-

(a) production is simple & less expensive.

(b) It is not effected by R, L, C components.


(c) They result in less losses in transformers

(e) Mesh:- A Mesh is a closed path during a circuit which doesn't contain any other closed path in it.

(f) Supernode:- A theoretical model in which two ref. nodes are considered having an ideal voltage source present b/w them as a single node.

(g) Phase difference:- It is difference in phase angle b/w two sinusoids or phasors.

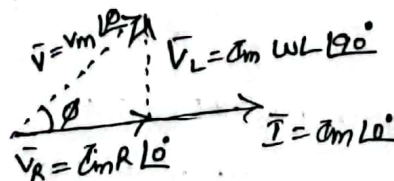(h) phasor diagram for series RL circuit:-



(1)

(i) Compensation Theorem:-

The resistance of any N/w can be replaced by a voltage source, having same voltage as voltage drop across resistance which is replaced.

(j) Condition for Max power transfer in Max power transfer Theorem:-

For DC ckt $R_L = R_S$

for AC ckt $Z_L = Z_S^*$

(k) Tellegen's Theorem:- Sum of instantaneous power consumed by various elements in various branches is zero for any N/w.

(l) $Z = R$ at resonance.

(m) Bandwidth = $\frac{f_{91}}{f_2 - f_1}$

(n) quality factor = Q electric energy stored in circuit divided by energy dissipated in one period.


UNIT-I

(2a) KCL + KVL with an example:- 7M.

State term:- (4M)

(3M) Interpret & example

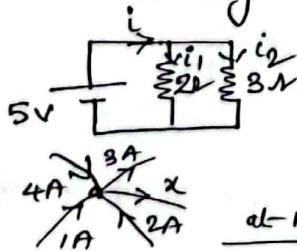KCL:- Algebraic sum of currents entering and exiting a node must equal zero.




$$i_1 = (2/5)A; \quad i_2 = (3/5) = \frac{5}{3}A$$

$$= \frac{5}{2} = 2.5A$$

$$i = i_1 + i_2 = 2.5 + 5/3 = 4.16A$$

at node:- $1 + 2 + 4 = 3 + x; \quad x = 7 - 3 = 4A$

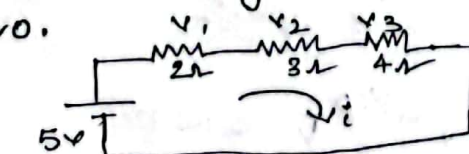KVL:- Algebraic sum of voltages around a closed path is zero.



$$V = V_1 + V_2 + V_3 = 45/9 = 5V$$

Hence proved.

$$i = \frac{5}{9}A;$$

$$V_1 = iR_1 = 5/9 \times 2 = 10/9V$$


$$V_2 = iR_2 = 3 \times 5/9 = 15/9V$$

$$V_3 = iR_3 = 4 \times 5/9 = 20/9V$$

(2b) Source current in N/w using Δ - Δ transformation:- (7M)

Solution procedure steps $\rightarrow$ 4M.

Formulae $\rightarrow$ 2M Answer:- 1M.

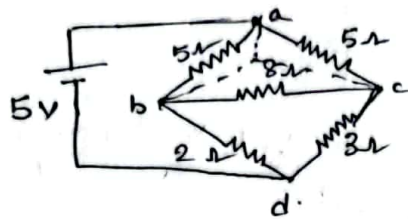


converting abc Δ to Δ

$$R_A = \frac{R_1 R_2}{R_1 + R_2 + R_3} \quad R_B = \frac{R_2 R_3}{R_1 + R_2 + R_3}$$

$$R_C = \frac{R_1 R_3}{R_1 + R_2 + R_3} \quad R_1 = 5 \quad R_2 = 5 \quad R_3 = 8$$

By Transforming $\rightarrow$

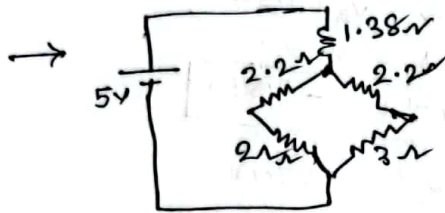

$$I = \frac{5}{3.71} = 1.347A$$

(2a) Average & RMS value for given waveform:- (7M)

Formulae:- (3M) Procedure & sol:- 4M.



$$v(t) = 10 \quad 0 < t < 1$$

$$= 0 \quad 1 < t < 2$$

$$V_{avg} = \frac{1}{T} \int_0^T v(t) dt = \frac{1}{2} \int_0^1 10 dt + 0 = \frac{10}{2} = 5V$$


$$V_{rms} = \sqrt{\frac{1}{T} \int_0^T v(t)^2 dt} = \sqrt{\frac{1}{2} \int_0^1 100 dt} = \sqrt{\frac{100}{2}} = 7.071V$$

(3b) Z_1, Z_2, Z_3 imp given in series + 1kel ckt:- (7M)

cal P, Q, $\cos \phi$

Formulae:- (3M)

Procedure & sol:- (4M)

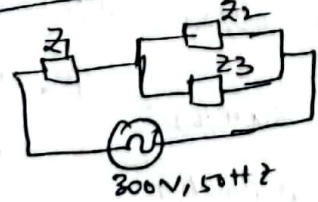

$$Z_1 = 6 + j8 \Omega; \quad Z_2 = 10 + j6 \Omega$$

$$Z_3 = 8 + j10 \Omega;$$

$$Z_2 || Z_3 = 4.7 + j4.04 \Omega; \quad Z_1 + (Z_2 || Z_3) = 16.1 \angle 48.36^\circ \Omega.$$

$$I = \frac{V}{Z} = \frac{300}{16.1 \angle 48.36} = 18.6 \angle -48.36$$

$$P = VI \cos \phi = 300 \times 18.6 \times \cos(48.36) = 3.71 kW$$


$$Q = VI \sin \phi = 300 \times 18.6 \times \sin(48.36) = 4.17 kVAR$$

$$\cos \phi = \cos(48.36) = 0.664$$

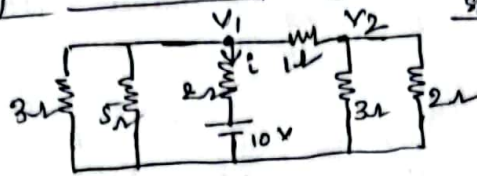(3)

UNIT-II

(4a) Mag of current drained from source 10V:- (7M)
Steps:- 4M sol:- 3M.



by app nodal analysis:- $V_1/3 + V_1/5 + \frac{V_1 - 10}{2} + \frac{V_1 - V_2}{1} = 0$;
 $2.03 V_1 - V_2 = 5$ (1)

$\frac{V_2 - V_1}{1} + \frac{V_2}{3} + \frac{V_2}{2} = 0$; $-V_1 + 1.83 V_2 = 0$; (2)


By solving (1) + (2)

$$V_1 = 3.36 V, V_2 = 1.84 V$$

Current drained by source.

$$i = \frac{V_1 - 10}{2} = -3.316 A$$

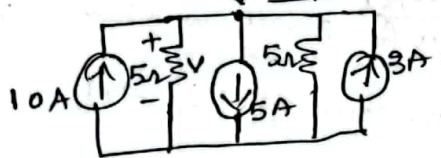(4b) Det V in circuit shown in fig:- (7M)
Steps:- 5M; sol:- 2M



By applying Nodal analysis


$$-10 + \frac{V}{5} + 5 + \frac{V}{5} - 3 = 0$$

$$-10 + 0.2V + 5 + 0.2V - 3 = 0$$

$$0.4V = 8; \quad V = \frac{8}{0.4} = 20V$$

OR

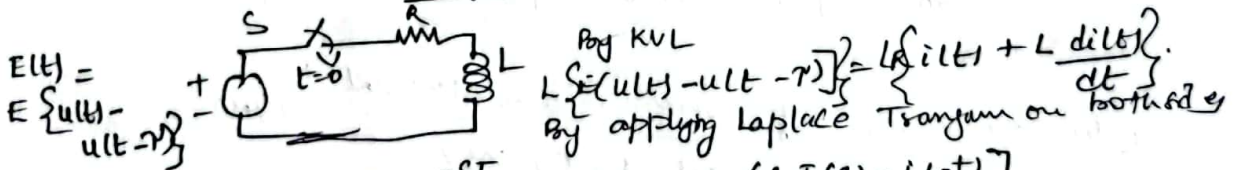(5a) RL series ckt with pulse excitation:- (7M)
Diagram:- (2M) Analysis + Steps:- (5M)



By KVL

$$L \frac{di(t)}{dt} + Ri(t) = E[u(t) - u(t - T)]$$

By applying Laplace Transform on both sides

$$E/s - E/s e^{-sT} = R I(s) + L (s I(s) - i(0^+))$$

as $i(0^+) = 0$

$$E/s (1 - e^{-sT}) = R I(s) + s L I(s); \quad I(s) = \frac{E(1 - e^{-sT})}{R(R + sL)}$$

$$= (1 - e^{-sT}) \cdot \frac{E}{L} \cdot \frac{1}{s(s + R/L)} = \frac{(1 - e^{-sT}) E}{L} = \frac{A}{s} + \frac{B}{s + R/L}$$

by solving using P. Fractions

$$A = E/R, \quad B = -E/R$$


$$\text{Then } L^{-1} \left\{ \frac{E}{s} (1 - e^{-sT}) \right\} = L^{-1} \left\{ \frac{E}{R} \left(\frac{1}{s} - \frac{e^{-sT}}{s} \right) \right\} = \frac{E}{R} (1 - e^{-sT})$$

$$i(t) = \frac{E}{R} u(t) - \frac{E}{R} u(t - T) - \frac{E}{R} e^{-R/L t} + \frac{E}{R} e^{-R/L (t - T)}$$


(4)

(5b) Find power absorbed by each element:- (7M)

Procedural steps:- (5M) $R_{01} = 2M$.

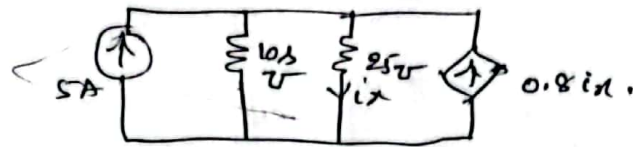

Transforming conductances to resistors

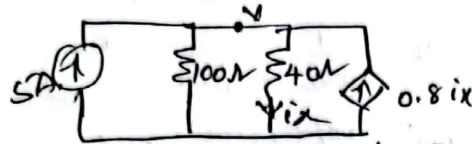

By Nodal analysis.

$$\frac{V}{100} + \frac{V}{40} = 5 + 0.8 \frac{V}{40}$$

$$0.015V = 5; \quad V = 333.33V$$

$$P_{\text{absorbed by source}} = (333.3)(-5) = \boxed{-1.66kW}$$

$$P_{100\Omega} = \frac{V^2}{R} = \frac{333.33^2}{100} = \boxed{1.11kW}$$

$$P_{40\Omega} = \frac{V^2}{R} = \frac{333.33^2}{40} = \boxed{2.77kW}$$

$$i_x = \frac{333.33}{40} = 8.33$$

$$P_{\text{Dep Source}} = (-0.8i_x) \times V = 0.8 \times 8.33 \times 333.33$$

$$P_{\text{Dep.}} = \boxed{-2.22kW}$$

UNIT-III

(6a) Thevenin's Theorem:- Advantages:- (2M) -4M.
(2M)

Thevenin's theorem:- Any linear circuit can be simplified, irrespective of how complex it is, to an equivalent circuit with a single voltage source and a series resistance.

Advantages:- ① used in analyzing linear ckt only & in power systems also.

② used in source modelling;

③ used in resistance measurement using wheatstone bridge.


④ reduces a complex circuit to a simple ckt.

⑤ It enables us to know action of o/p part directly.

(6b) Max power transfer theorem proof for DC & AC excitation:- (10M)

DC excitation proof:- 5M AC excitation proof:- (5M)

Proof:-

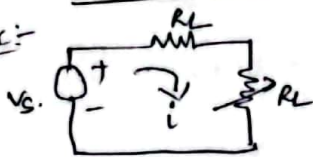

$$I = \frac{V_S}{R_S + R_L}$$

$$P_{R_L} = I^2 R_L = \frac{V_S^2 R_L}{(R_S + R_L)^2}$$


$$\frac{dP}{dR_L} = 0; \quad \frac{d}{dR_L} \left[\frac{V_S^2 R_L}{(R_S + R_L)^2} \right]$$

$$\frac{V_S^2 ((R_S + R_L)^2 - 2R_L(R_S + R_L))}{(R_S + R_L)^4} = 0$$

$$\therefore (R_S + R_L)^2 - 2R_L(R_S + R_L) = 0$$

$$\therefore \boxed{R_S = R_L}$$

for AC:-

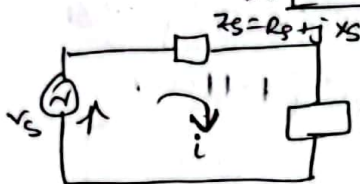


$$I = \frac{V_S}{(R_S + jX_S) + (R_L + jX_L)}$$

$$|I| = \frac{V_S}{\sqrt{(R_S + R_L)^2 + (X_S + X_L)^2}}$$


$$P = I^2 R_L = \frac{V_S^2 R_L}{(R_S + R_L)^2 + (X_S + X_L)^2}$$

if R_L is fixed the value of P maximum when $\boxed{X_S = -X_L}$
i.e. $\boxed{Z_L = Z_S^*}$

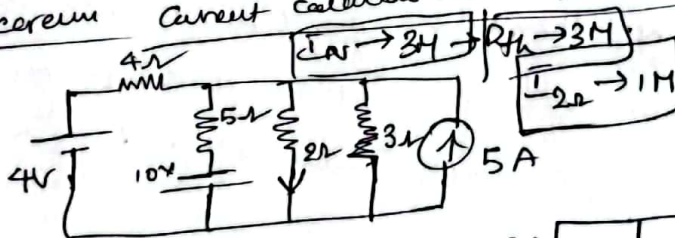(OR)
⑦a) Norton's Theorem Current calculation through 2Ω res:- (7M)




for I_N :-

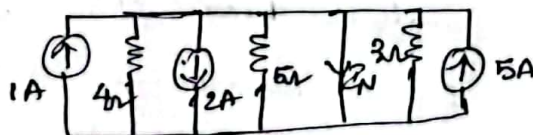

$$\text{Hence } \boxed{I_N = 3A}$$

open circuit sources + short ckt in H source and disconnect load.

for R_N :-

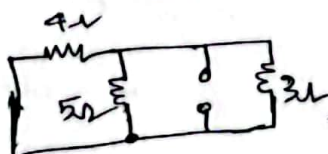

$$R_N = (4 || 5 || 3) = \boxed{1.276\Omega}$$

Current through 2Ω load



$$I_L = \frac{3 \times 1.276}{2 + 1.276}$$


$$\boxed{I_L = 1.768A}$$

七


voltage across $10\ \Omega$ using superposition theorem

First Some actrogalors :- 3M

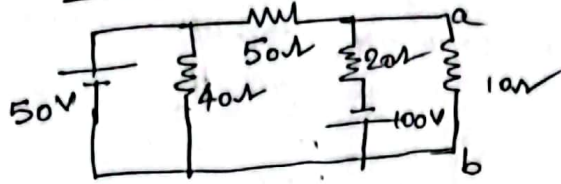second source activity = 304 $\frac{101}{\text{August}}$ 14.




First source Acting alone:-

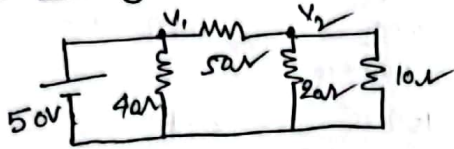

$$v_1 = 50; \quad \frac{v_2 - v_1}{50} + \frac{v_2}{20} + \frac{v_2}{10} = 0.$$

hiring $V_2 = 5.88\%$

second time asking about:-

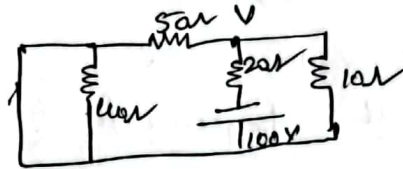

$$\frac{V}{50} + \frac{V+100}{20} + \frac{V}{10} = 0;$$

$$0.02V + 0.05V + 0.1V = 0;$$

$$0.17V = -5$$


$$V = \frac{-5}{0.17} = -29.41V.$$

$$V = V_1 + V_2 = 5.88 - 29.41 = -23.53 \text{ V}$$

UNIT - IV

Q2) Band width of series RLC circuit :- (7M)

Diag: 2M Procedure 4801 5M

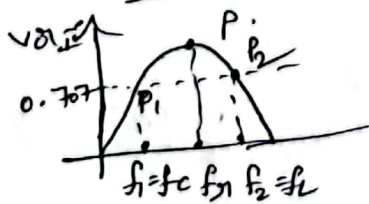

Bandwidth of system is range of f for which amplitude is equal to -70% of its value at res. frequency.

$$B.W = f_2 - f_1$$

Hence $\frac{1}{w_{1c}} - \frac{w_{1L}}{L_1} = R; \quad w_{2L} - \frac{1}{w_{2c}} = R; \rightarrow (2)$

$1 = 2$; $\frac{1}{w_1 c} - w_1 L = w_2 L - \frac{1}{w_2 c} \rightarrow L(w_1 + w_2) = \frac{1}{c} \left(\frac{w_1 + w_2}{w_1 w_2} \right)$;
 $w_1 w_2 = \frac{1}{c}$; $w_1 = \frac{1}{c w_2}$; $w_1 = w_1, w_2$

$$\text{add } ① + ② \quad \frac{1}{\omega_c} - \omega_{1c} + \omega_{2c} - \frac{1}{\omega_c} = 22;$$

$$(w_2 - w)L + \frac{1}{c} \left(\frac{w_2 - w}{w_1 w_2} \right) = 2R, \quad \therefore c = \frac{1}{w_1 w_2}; \quad w_1 w_2 = w_3^2$$

$$(w_2 - w_1)k + \alpha_2 \sqrt{L} \frac{(w_1 - w_2)}{w_2 \sqrt{r}} = 2R_2 \cdot \frac{1}{2\pi L} \cdot \boxed{f_2 - f_1 = R/2\pi L} \quad \text{and } B \cdot w = R/2\pi L$$

7


86

series RLC ckt Resonance $\rightarrow$ (7M).

f_n Q. f B.W $\rightarrow$ formula $\rightarrow$ 4M.

Solⁿ (6M)

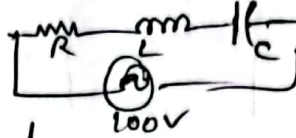$R = 1K\Omega$; $L = 100mH$; $C = 10\mu F$; $V = 100V$




$$f_n = \frac{1}{2\pi\sqrt{LC}} = \frac{1}{2\pi\sqrt{(100 \times 10^{-3})(10 \times 10^{-6})}} = 159.15 \text{ Hz}$$

$$B.W = \frac{R}{2\pi L} = \frac{1000}{2\pi \times 100 \times 10^{-3}} = 1.59 \text{ KHz}$$

$$Q \text{ f} = \frac{f_n}{B.W} = \frac{159.15}{1.59 \times 10^3} = 0.1$$

(OR)

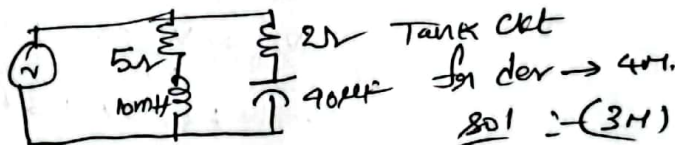
90) Resonant frequency for given circuit $\rightarrow$



f_n der $\rightarrow$ 4M.

Solⁿ $\rightarrow$ (3M)

Derⁿ $\rightarrow$

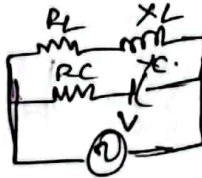

$$Y = \frac{1}{Z_L} + \frac{1}{Z_C}; \quad Z_L = R_L + j\omega L \quad Z_C = R_C - j/\omega C$$

$$Y = \frac{1}{R_L + j\omega L} \times \frac{R_L - j\omega L}{R_L - j\omega L} + \frac{1}{R_C - j/\omega C} \times \frac{R_C + j/\omega C}{R_C + j/\omega C}$$

$$Y = \frac{R_L - j\omega L}{R_L^2 - j^2\omega^2 L^2} + \frac{R_C + j/\omega C}{R_C^2 - j^2/\omega^2 C^2}$$

extracting imaginary part & set resonance net susceptance is zero.

$$\frac{1/\omega C}{R_C^2 + 1/\omega^2 C^2} - \frac{\omega L}{R_L^2 + \omega^2 L^2} = 0$$

By simplifying $\omega_0^2 (R_C^2 - 4C) = \frac{1}{LC} (R_L^2 - 4C)$


$$\omega_0^2 = \frac{1}{LC} \left[\frac{R_L^2 - 4C}{R_C^2 - 4C} \right]$$

$$\therefore f_n = \frac{1}{2\pi\sqrt{LC}} \left[\frac{R_L^2 - 4C}{R_C^2 - 4C} \right]^{1/2}$$

By sub $R_L = 5\Omega$; $L = 10mH$; $R_C = 2\Omega$; $C = 40\mu F$ + simplifying.

$$f_n = 240.5 \text{ Hz}$$

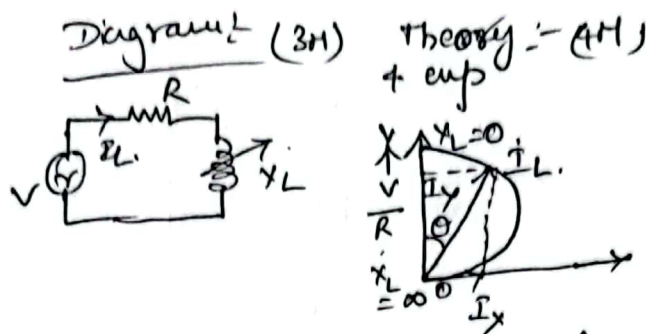(9b) Current locus diag of RL series ckt with X_L variable parameter :- (7M)



when $X_L = 0$, I_L assumes $\frac{V}{R}$ & $\theta = 0$; $Pf = 1$

as $X_L \uparrow$, from zero, I_L is reduced and finally when X_L is ∞ , current becomes zero and θ will be lagging behind voltage by 90° as shown in fig. Current vector describes a semi circle with diameter $\frac{V}{R}$ and lies in right hand side of volt vector OV. The active comp of current $OI_L \cos \theta$ is proportional to power consumed in RL circuit.

eqn. of circle; $Z_R^2 + Z_Y^2 = \frac{V^2}{R^2 + X_L^2}$

$Z^2 = R^2 + X_L^2 = \frac{V^2}{I_L^2}$; $Z_R^2 + Z_Y^2 = \frac{V^2}{I_L^2}$

$Z_R^2 + Z_Y^2 - \frac{V^2}{I_L^2} = 0$

$Z_R^2 + \left(Z_Y - \frac{V}{I_L}\right)^2 = \left(\frac{V}{2I_L}\right)^2$

Radius is $\frac{V}{2R}$; and Centroid is $0, \frac{V}{2R}$

X X THE END X X

Sig of Staff:-

(1) Dr. N. Kavitik

Prof

Assoc Prof in Dept of EEE

Dr. N. Renu Devi

Prof & Head, Dept of EEE

Sig of HOD of

Dept of EEE

(1) Dr. N. Renu Devi

Prof & Head,

Dept of EEE

Head of the Department,
Electrical & Electronics Engg.
Bapatla Engineering College
BAPATLA - 522101.