

Hall Ticket Number:

--	--	--	--	--	--	--	--	--

II/IV B.Tech (Regular\Supplementary) DEGREE EXAMINATION

July/August, 2022

Electrical and Electronics Engineering

Fourth Semester

Digital Electronics

Time: Three Hours

Maximum: 70 Marks

Answer Question No.1 compulsorily.

(1X14 = 14 Marks)

Answer ONE question from each unit.

(4X14=56 Marks)

- | | | | | |
|-----------------|--|-----|----|-----|
| 1 | a) Represent 248 ₁₀ in BCD | CO1 | L1 | 1 |
| | b) What is ODD parity. | CO1 | L1 | 1 |
| | c) State distributive law. | CO1 | L2 | 1 |
| | d) Obtain Truth Table for EX-OR gate. | CO2 | L2 | 1 |
| | e) Write the truth table of Full Adder. | CO2 | L2 | 1 |
| | f) What is comparator | CO2 | L1 | 1 |
| | g) What is decoder | CO2 | L1 | 1 |
| | h) What are the applications of Multiplexer | CO3 | L2 | 1 |
| | i) Define race around condition. | CO3 | L1 | 1 |
| | j) What is toggling. | CO3 | L3 | 1 |
| | k) Draw the circuit of SR flip flop. | CO4 | L3 | 1 |
| | l) What are the different types of shift registers? | CO6 | L2 | 1 |
| | m) What are the different types of A/D converters? | CO5 | L2 | 1 |
| | n) What is PLD? | CO6 | L2 | 1 |
| Unit-I | | | | |
| 2 | a) Obtain the 1's complement and 2's complement of the binary numbers
i. 1010111 ii. 0111001 iii. 1001 iv. 00010 | CO1 | L2 | 7M |
| | b) Construct the hamming code for 7 bit data bits 1011011. | CO1 | L4 | 7M |
| (OR) | | | | |
| 3 | a) Briefly explain different logic circuits with Truth tables and logic symbols. | CO1 | L2 | 7M |
| | b) Briefly explain TTL logic family with neat sketches. | CO1 | L2 | 7M |
| Unit-II | | | | |
| 4 | a) Simplify the following using K-Map
$F = m(0, 1, 2, 3, 8, 9, 10, 14, 15)$ | CO2 | L4 | 7M |
| | b) Design 3 bit excess 3 code to gray code converter. | CO2 | L2 | 7M |
| (OR) | | | | |
| 5 | a) Design 4 bit serial adder/subtractor with control input M? | CO3 | L3 | 7M |
| | b) Design and explain 8*1 MUX. | CO3 | L2 | 7M |
| Unit-III | | | | |
| 6 | a) Convert the following flip-flops with excitation table
a) SR to D flip - flop
b) JK to D flip - flop | CO4 | L4 | 14M |
| (OR) | | | | |
| 7 | a) Design a 4 bit synchronous counter with D flip - flops and explain its working. | CO6 | L4 | 7M |
| | b) Design a bidirectional shift register. | CO6 | L3 | 7M |
| Unit-IV | | | | |
| 8 | a) Draw and explain about Sample and Hold circuit. | CO5 | L2 | 7M |
| | b) Discuss about successive approximation A/D converter. | CO5 | L2 | 7M |
| (OR) | | | | |
| 9 | Implement the following function using PLA and PAL:
a. $f_1(A, B, C, D) = \sum(0, 1, 2, 3, 6, 9, 11)$
b. $f_2(A, B, C, D) = \sum(0, 1, 6, 8, 9)$ | CO6 | L4 | 14M |

1.

a) 248_{10} in BCD 0010 0100 1000

b) If number of ones are odd number in data bits, then it is called odd parity.

c) $A + BC = (A + B)(A + C)$

d)

A	B	C
0	0	1
0	1	0
1	0	0
1	1	1

e)

A	B	C	S	C
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1


f) which compares magnitude of two bits is called comparator.

g) A decoder is a combinational circuit that converts binary information from n input lines to a maximum of 2^n unique output lines.

- h)
1. data selector device
 2. communication systems
 3. telephone networks

 i) When both inputs of JK flip flop are one, the output is uncertain. This condition of JK flip flop is called race around condition.

j) In T flip flop, when the both inputs are 1, the next output state is changed with the complement of the present state output. This process is known as "toggling".



- l)
- 1) left shift register
 - 2) Right shift register

- m) 1. Successive approximation type
2. Dual slope ADC.

n) PLD is programmable logic devices are the integrated circuits. They contain an array of AND gates and another array of OR gates.

UNIT-1

2)

a)

i) 1010111

1's Complement - 0101000 } 2M

2's Complement - 0101001

ii) 0111001

1's Complement - 1000110 } 2M

2's Complement - 1000111

iii) 1001

1's Complement - 0110 } 1M

2's Complement - 0111

iv) 00010

1's Complement - 11101 } 2M

2's Complement - 11110

b)

Given data bits = 1011011

$$\text{no. of parity bits} \Rightarrow 2^P \geq m + P + 1$$

Here $m = 7$ (data bits)

$\therefore$ for $P = 4$, above equation will satisfy.

$$\therefore \text{no. of parity bits} = 4$$

$$\text{no. of data bits} = 7$$

$$\therefore \text{length of Hamming code} = m + P = 7 + 4 = 11.$$

0001	0010	0011	0100	0101	0110	0111	1000	1001	1010	1011
P_1	P_2	m_1	P_3	m_2	m_3	m_4	P_4	m_5	m_6	m_7
1	2	3	4	5	6	7	8	9	10	11
-	-	1	-	0	1	1	-	0	1	1

Here i'm considering even parity / odd parity.

$$C_1 = P_1 m_1 m_2 m_4 m_5 m_7$$

$$= - 1 0 1 0 1$$

for even parity, $P_1 = 1$

for odd parity, $P_1 = 0$

$$C_2 = P_2 m_1 m_3 m_4 m_6 m_7$$

$$= - 1 1 1 1 1$$

for even parity, $P_2 = 1$

for odd parity, $P_2 = 0$

$$C_3 = P_3 m_2 m_3 m_4$$

$$= - 0 \ 1 \ 1$$

for even parity, $P_3 = 0$

for odd parity, $P_3 = 1$

$$C_4 = P_4 m_5 m_6 m_7$$

$$= - 0 \ 1 \ 1$$

for even parity, $P_4 = 0$

for odd parity, $P_4 = 1$

$\therefore$ For even parity, the hamming code is,

1 1 1 0 0 1 1 0 0 1 1

for odd parity, the hamming code is,


0 0 1 1 0 1 1 1 0 1 1

(OR)

3)

- a) 1) OR logic : It performs addition operation.
when any one of the input is high, then the output is high. If both the inputs are low, then the output is low.

logic diagram

 


Truth table

A	B	C
0	0	0
0	1	1
1	0	1
1	1	1

- 2) AND logic : It performs ~~addition~~ ^{multiplication} operation. when any one of the input is low, then the output is low.

logic diagram

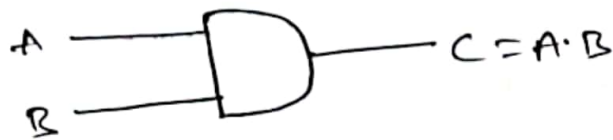

Truth Table } 1M

A	B	C
0	0	0
0	1	0
1	0	0
1	1	1

- 3) NOT logic : It performs Complement operation.


logic diagram



Truth Table } 1M

A	C
0	1
1	0

 
- 4) NAND logic : The combination of AND gate and NOT gate is called NAND.



Truth Table } 1M

A	B	C
0	0	1
0	1	1
1	0	1
1	1	0

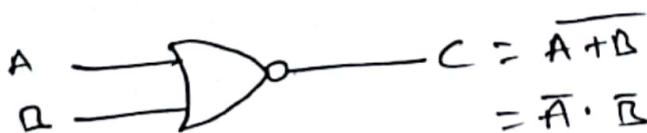
- 5) NOR logic : The combination of OR gate and NOT gate is called NOR.



Truth Table } 1M

A	B	C
0	0	1
0	1	0
1	0	0
1	1	0

 6) Ex-OR logic : If the both inputs are same then only output is high.




Truth table

A	B	C
0	0	1
0	1	0
1	0	0
1	1	1

} 1M

 7) Ex-NOR logic : If the both inputs are different, then only output is high.




Truth table

A	B	C
0	0	0
0	1	1
1	0	1
1	1	0

} 1M

b)

 

TTL stands for transistor transistor logic. From the above diagram, the transistor T_1 has two emitters to allow two inputs into the transistor. Now, as connected the base voltage will be at 5V. If both the inputs are at logic 1, the potential difference across the base and emitter would be zero or nearly. Hence no current will flow

and the transistor is turned off. So the collector voltage would also be equal to about 5V. Hence this potential can drive current through the emitter of the transistor T_2 . This then allows the collector voltage of the transistor T_2 to fall. Now, due to the current flowing through the emitter, there would be a voltage drop across the resistor R_3 . The desired voltage drop would be 0.7V. As seen this is the input of transistor T_3 . Hence the transistor is turned on. Due to saturation the collector voltage will fall about 0.2V which is logic 0. } 2M

For the transistor T_4 , observe that the emitter voltage is made up of the entire voltage of the transistor T_2 plus the voltage drop across the diode D about 0.7V. Now the base voltage of transistor T_4 would be the voltage across base emitter of the T_2 and the voltage of the entire transistor across emitter collector.

UNIT - II

4)

a)

AB \ CD					
	00	01	11	10	
00	1	1	1	1	①
01					
11			1	1	③
10	1	1		1	

} 4M

$$f_{min} = \textcircled{1} + \textcircled{2} + \textcircled{3} + \textcircled{4}$$

$$= \bar{A}\bar{B} + \bar{B}\bar{C} + ABC + AC\bar{D} \quad \} 2M$$

b)

X5-3 code Binary Gray code

A B C B₃ B₂ B₁ G₃ G₂ G₁

0	0	1	1	0	0	0	0	0	0	0
1	0	0		0	0	1	0	0	1	
1	0	1		0	1	0	0	1	1	
1	1	0		0	1	1	0	1	0	
1	1	1		1	0	0	1	1	0	

} 2M

Don't cares.

1	0	1
1	1	0
1	1	1

A \ BC	00	01	11	10
0	X	X		X
1			1	

$$G_1 = \sum m(4) + d(5, 6, 7)$$

$$G_3 = \sum m(7) + d(0, 1, 2)$$

$$G_3 = ABC$$

$$G_2 = \sum m(5, 6, 7) + d(0, 1, 2)$$

A \ BC	00	01	11	10
0	X	X		X
1		1	1	1

$$G_2 = AC + B\bar{C}$$

$$AC + AB$$


3M

$$G_3 = \sum m(4, 5) + d(0, 1, 2)$$


A \ BC	00	01	11	10
0	X	X		X
1	1	1		

$$G_3 = \bar{A}$$

(5)

 

(OR)

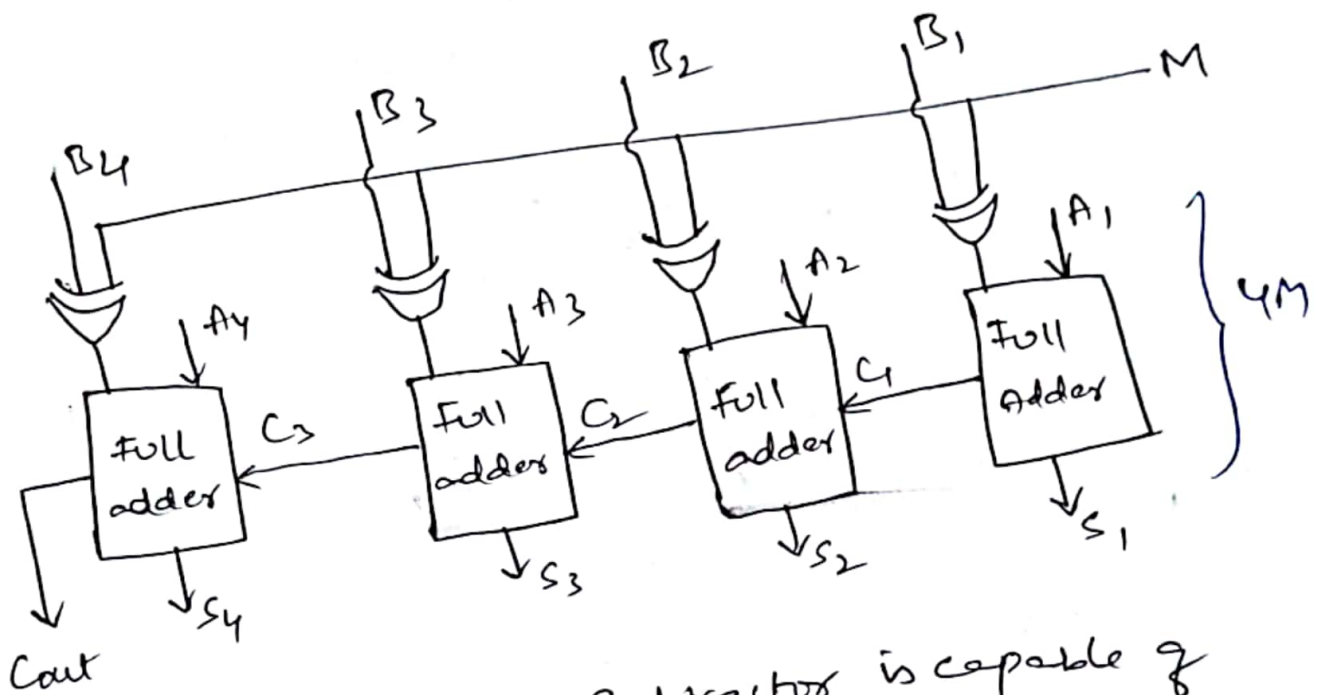


A Binary adder Subtractor is capable of both the addition and subtraction of binary numbers in one circuit itself.

Here we are using one extra input called Mode Control input. When mode control input is 1, circuit acts as adder and when it is 0, circuit acts as subtractor. The final output of the circuit is Cout S₄S₃S₂S₁.

5)

 b) An 8×1 Mux consists of eight data inputs D_0 through D_7 , three input select lines S_0 through S_2 and a single output line Y . Depending on the select lines combinations, multiplexer selects the inputs.



The truth table of 8×1 Mux is,

Selection inputs			output (Y)
S_2	S_1	S_0	
0	0	0	D_0
0	0	1	D_1
0	1	0	D_2
0	1	1	D_3
1	0	0	D_4
1	0	1	D_5
1	1	0	D_6
1	1	1	D_7

3M

UNIT - III

b)

a)

SR to D Flip flop:

available flip flop = SR

Required = D

Characteristic table of D flip flop is,

Q_n	D	Q_{n+1}
0	0	0
0	1	1
1	0	0
1	1	1

3M

Excitation table of SR flip flop is,

Q_n	Q_{n+1}	S	R
0	0	0	X
0	1	1	0
1	0	0	1
1	1	X	0

from excitation table extend the characteristic table.

Q_n	D	Q_{n+1}	S	R
0	0	0	0	X
0	1	1	1	0
1	0	0	0	1
1	1	1	X	0

3M

$$S = \sum m(1) + d(3)$$

RCE




$$S = \overline{Q_n} D$$

$$R = \sum m(2) + d(0)$$

$\Phi_n \backslash D$	0	1
0	X	
1	1	

$R = \bar{D}$

Required D flip flop is,

 

JK to D flip flop

Available flip flop = JK
Required = D

Characteristic table of D flip flop is,

Φ_n	D	Φ_{n+1}
0	0	0
0	1	1
1	0	0
1	1	1

Excitation table of JK flip flop is,

Φ_n	Φ_{n+1}	J	K
0	0	0	X
0	1	1	X
1	0	X	1
1	1	X	0

From excitation table, extend the characteristic table,

Q_n	D	Q_{n+1}	J	K
0	0	0	0	x
0	1	1	1	x
1	0	0	x	1
1	1	1	x	0

$$J = \sum m(1) + d(2,3)$$

Q_n	D	0	1
0			1
1		x	x


$J = D$

$$K = \sum m(2) + d(0,1)$$

Q_n	D	0	1
0		x	x
1		1	

$K = \bar{D}$

∴ Required flip flop is,

 

(OR)

7)

9)

Here 4 bits $\Rightarrow$ 4 flip flops required.
excitation table of D-flip flop is,

Q_n	Q_{n+1}	D
0	0	0
0	1	1
1	0	0
1	1	1

1M

Q_A	Q_B	Q_C	Q_D	Q_A^+	Q_B^+	Q_C^+	Q_D^+	D_A	D_B	D_C	D_D
0	0	0	0	0	0	0	1	0	0	0	1
0	0	0	1	0	0	1	0	0	0	1	0
0	0	1	0	0	0	0	1	0	0	0	1
0	0	1	1	0	0	1	0	0	1	0	0
0	1	0	0	0	0	1	0	0	1	1	0
0	1	0	1	0	0	1	1	0	1	1	1
0	1	1	0	0	0	1	1	1	0	0	0
0	1	1	1	0	0	1	0	1	0	0	1
1	0	0	0	1	1	0	0	1	0	0	1
1	0	0	1	1	1	0	1	1	0	1	0
1	0	1	0	1	1	0	1	1	0	1	1
1	0	1	1	1	1	0	0	1	0	1	0
1	1	0	0	1	1	1	0	1	1	0	1
1	1	0	1	1	1	1	1	1	1	1	0
1	1	1	0	1	1	1	1	1	1	1	1
1	1	1	1	1	1	1	1	1	1	1	1

2M

$$D_A = \sum m(7, 8, 9, 10, 11, 12, 13, 14)$$

		$Q_C Q_D$			
		00	01	11	10
$Q_A Q_B$	00				
	01			1	
	11	1	1		1
	10	1	1	1	1

$$D_A = Q_A \bar{Q}_B + Q_A \bar{Q}_C + Q_A \bar{Q}_D + \bar{Q}_A Q_B Q_C Q_D$$

$$D_B = \sum m(3, 4, 5, 6, 11, 12, 13, 14)$$

		$Q_C Q_D$			
		00	01	11	10
$Q_A Q_B$	00			1	
	01	1	1		1
	11	1	1		
	10			1	

$$D_B = Q_B \bar{Q}_C + Q_B \bar{Q}_D + \bar{Q}_B Q_C Q_D$$

$$D_C = \sum m(1, 2, 5, 6, 9, 10, 13, 14)$$

		$Q_C Q_D$			
		00	01	11	10
$Q_A Q_B$	00		1		1
	01		1		1
	11		1		1
	10		1		1



$$D_C = \bar{Q}_C Q_D + Q_C \bar{Q}_D$$

$$D_D = \sum m(0, 2, 4, 6, 8, 10, 12, 14)$$

		$Q_C Q_D$			
		00	01	11	10
$Q_A Q_B$	00	1			1
	01	1			
	11	1			1
	10	1			1

$$D_D = \bar{Q}_D$$

27

  


A Bidirectional shift register is used for shifting the data in either left or right side based on the input. This register can be implemented through a D flip flop and logic gates which allow the data bit transfer from one stage to next stage to any side either right or left based on an input signal. Here the direction of data shifting depends upon the mode control input. 3M

Mode control input is a extra input used to choose the operation as left shift or right shift. If the mode control input is 1, then the register operates as right shift whereas if mode control input is zero, the register operates as left shift register.


Unit - IV

8)
a)

 

The main components which a Sample and Hold circuit involves is an N-channel Enhancement type MOSFET, a capacitor to store and hold electric charge and a high precision operational amplifier.


The N channel Enhancement MOSFET will be used a switching element. The input voltage applied through its drain terminal and Control voltage will be applied through its gate terminal. When the positive pulse of the control voltage is applied, the MOSFET will be switched to ON state and it acts as a closed switch. When the control voltage is zero then the MOSFET will be switched to off state and acts as open switch.

 

→ Input and output waveforms.

2M

b)

 

A Successive approximation type ADC produces a digital output which is, approximately equal to the analog input by using successive approximation technique internally.

The successive approximation type ADC mainly consists of 5 blocks — Clock signal generator, Successive approximation register (SAR), DAC, Comparator and Control logic.

The control logic resets all the bits of SAR and enables the clock signal generator in order to send the clock pulses to SAR. The binary data present in SAR will be updated for every clock pulse. The DAC converts the received digital input into an analog output. The comparator compares this analog value V_a with the external input value V_i . The output of comparator will be 1 as long as V_i is greater than V_a . The output of comparator is zero, when V_i is less than V_a .

(OR)

9)

$$f_1(A, B, C, D) = \sum m(0, 1, 2, 3, 6, 9, 11)$$

AB \ CD	00	01	11	10
00	1	1	1	1
01				
11				
10		1	1	

$$f_1(A, B, C, D) = \bar{A}\bar{B} + \bar{A}D + \bar{A}C\bar{B}$$

$$F_1(C) = \sum m(4, 5, 7, 8, 10, 12, 13, 14, 15)$$

AB \ CD	00	01	11	10
00				
01	1	1	1	1
11	1	1	1	1
10	1			1

$$F_1(C) = \bar{A}\bar{B} + A\bar{B} + B\bar{C} + BD$$

$$F_2(A, B, C, D) = \sum m(0, 1, 6, 8, 9)$$

AB \ CD	00	01	11	10
00	1	1		
01				1
11				
10	1	1		


$$F_2(A, B, C, D) = \bar{A}\bar{B} + \bar{A}B\bar{C}\bar{D}$$

$$F_2(C) = \sum m(2, 3, 4, 5, 7, 10, 11, 12, 13, 14, 15)$$

AB \ CD	00	01	11	10
00			1	1
01	1	1	1	1
11				1
10				1


$$F_2(C) = B\bar{C} + AC + \bar{A}C + BD$$

PLA Table

 

PAL Table

Here considering $F_1(c)$ & $F_2(c)$

 

Scene prepared by

1. Sai Goutham Adine
(8500588472)

2. M. Siva Ravi Krishna
(9700801417)

Kanishk
HOD, EEE Dept